

# – Fuji IGBT Module V Series 1700V Family –

## Parallel connection of 2in1 package modules

Circuit configuration and formula

$$\Delta V_{on} = |V_{on2} - V_{on1}| \quad (V_{on2} > V_{on1})$$

$$I_c(ave) = (I_1 + I_2) / 2$$

Current imbalance is caused by the difference between  $V_{on1}$  and  $V_{on2}$ , and current is divided into  $I_1$  and  $I_2$ . In this case, the current imbalance can be obtained from the following calculating formula.

$$\alpha = \left( \frac{I_1}{I_{C(ave)}} - 1 \right) \times 100 \quad (\%)$$

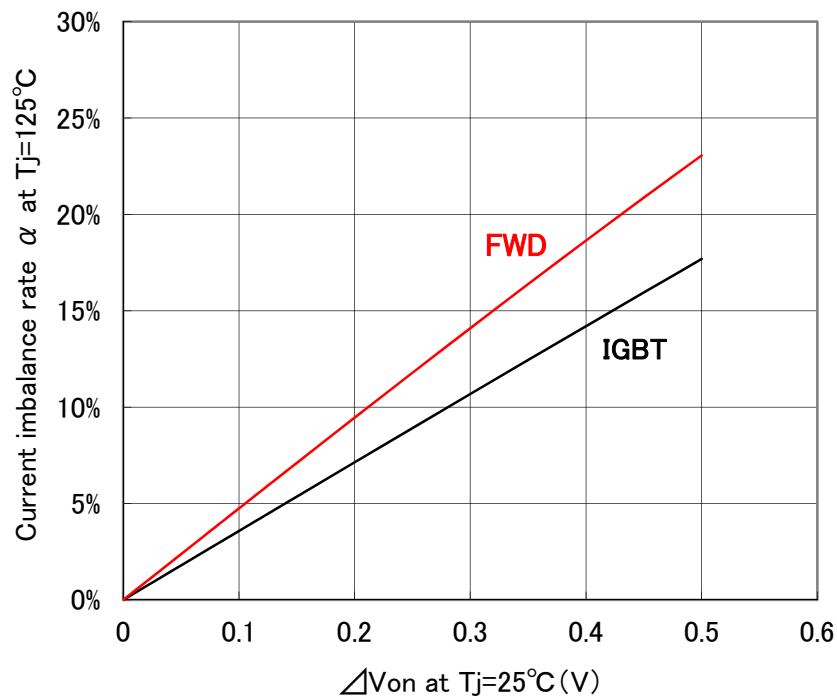
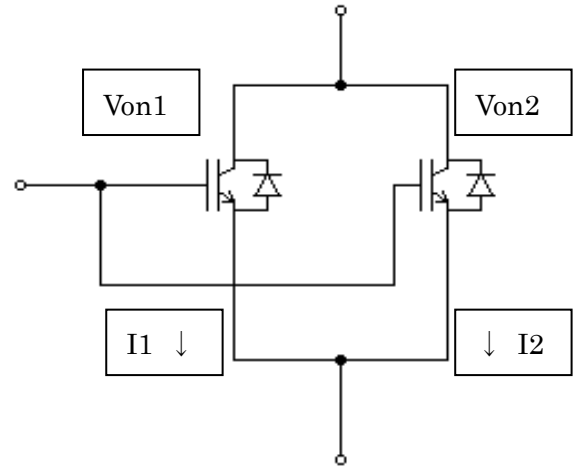


Fig. ΔVon and current imbalance rate

When  $n$  IGBT modules are connected in parallel, the maximum allowable current  $\Sigma I$  can be expressed in the following formula by using the current imbalance rate  $\alpha$  at two-parallel connection. This maximum allowable current  $\Sigma I$  is used for reference only.

$$\Sigma I = I_{C(max)} \left[ 1 + (n-1) \frac{\left(1 - \frac{\alpha}{100}\right)}{\left(1 + \frac{\alpha}{100}\right)} \right]$$