

# Power factor correction IC: FA1B00N

## Power supply design example: 390 V / 150 W

### Reference Design

#### 1. Overview


This document is a design example of PFC circuit using FA1B00N, critical conduction mode power factor correction IC. The rating output is 390V/150W.

#### 2. Features of FA1B00N

- ✓ Very Low Standby Power by disusing Input Voltage Detection Resistors
- ✓ High-precision over current protection:  $0.65\text{ V} \pm 2\%$
- ✓ Improved power efficiency at light load due to Maximum Frequency Limitation
- ✓ No Audible Noise at Startup by overshoot reduction circuit
- ✓ Low current consumption by CMOS process
- ✓ Start-up : 300  $\mu\text{A}$  (max.), Operating : 1.2 mA (typ.)
- ✓ Enabled to drive power MOSFET directly
  - Output peak current, source : 0.5 A, sink : 1 A
- ✓ Open/short protection at feedback (FB) pin
- ✓ Under-voltage Lockout, 13 V ON / 9 V OFF
- ✓ External signal-linked ON/OFF function built in FB pin



#### 3. Circuit diagram

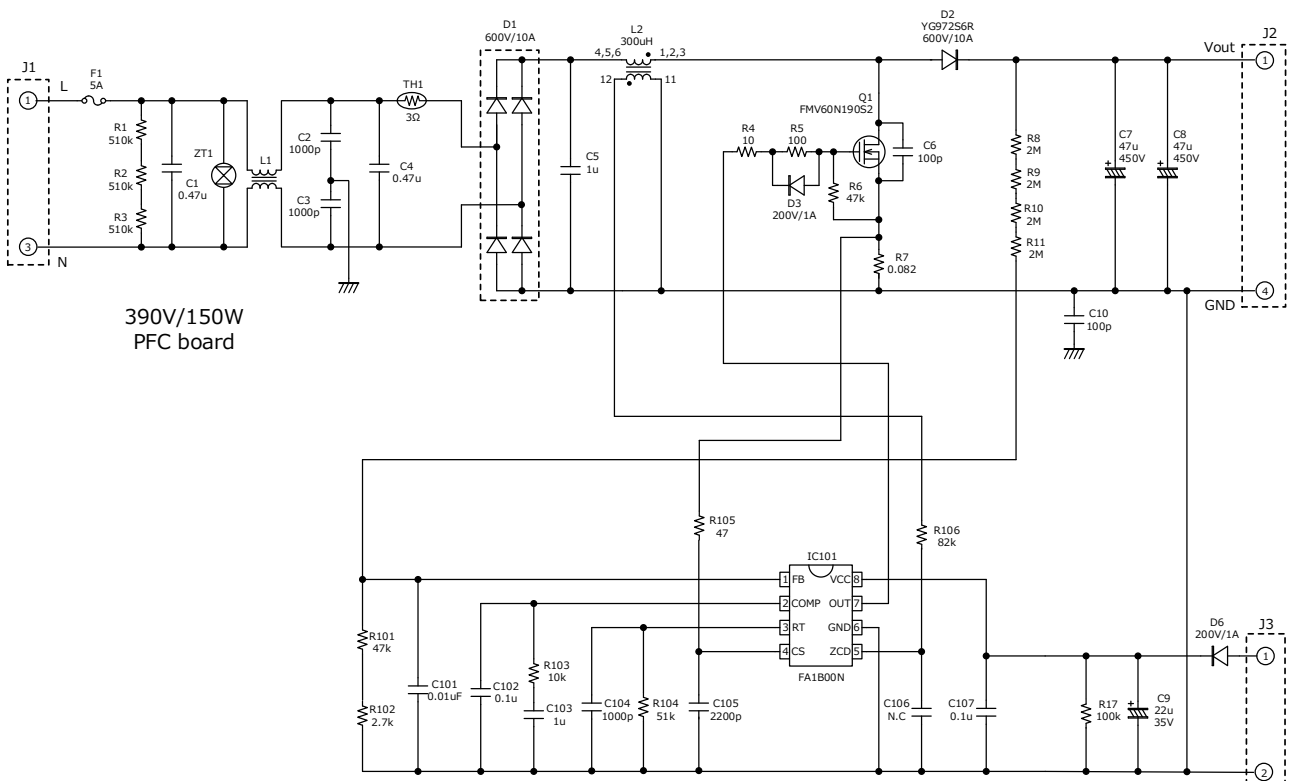

※ An external regulated power supply is connected to connector J3 and the supply voltage to VCC is 15 V.


### 4. Power supply specifications

| Item                | Value  | Unit |
|---------------------|--|------|
| Input voltage       | 90 to 264  | Vac  |
| Output voltage      | 390  | Vdc  |
| Output power        | 150  | W    |
| VCC supply voltage  | 15   | V    |
| Protection function | <ul style="list-style-type: none"> <li>◆ Overcurrent limiting of power MOSFET 【CS pin】</li> <li>◆ Overvoltage limiting 【FB pin】</li> <li>◆ Open/Short protection at FB pin</li> <li>◆ Overshoot reduction function 【COMP pin】</li> </ul> |      |

### 5. Start up characteristics of Power supply


This reference board improves the power factor by driving the IC with an external power supply. There are two ways to start it. ① Reference board is started up by turning on VCC after AC line is turned on. ② Reference board is started up by turning on AC line voltage after VCC is turned on.

#### ① Startup by turning on VCC

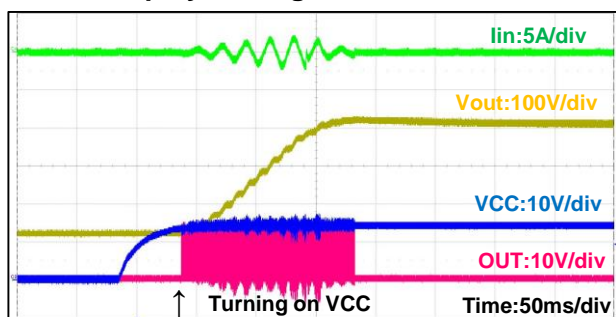

※IC operation started by VCC pin function

#### ② Startup by turning on AC input

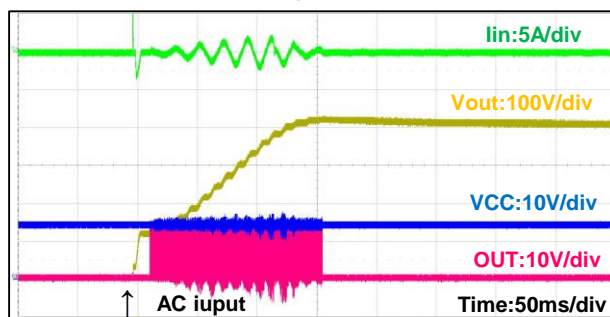



※IC operation started by FB pin function







Vac: 90V / 50Hz, lin: input current, Vout: output voltage, VCC: voltage at VCC pin, OUT: voltage at OUT pin
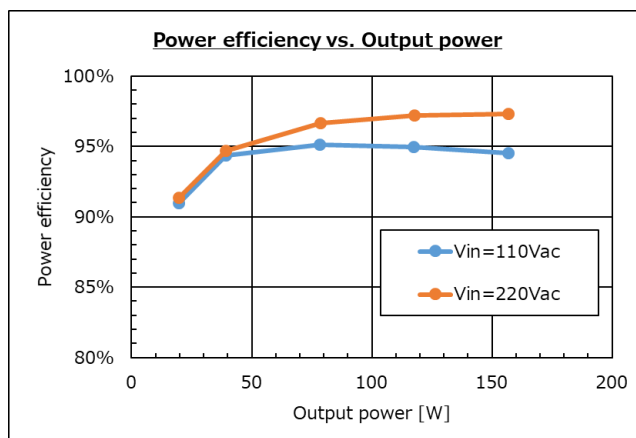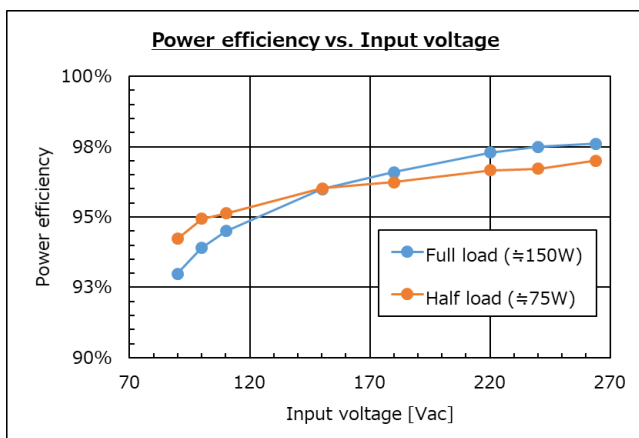
### 6. Electrical characteristics



The input / output characteristics of the reference board are as follows.

An 15V external regulated power supply is connected to connector J3. It is supplied to VCC pin of the IC.



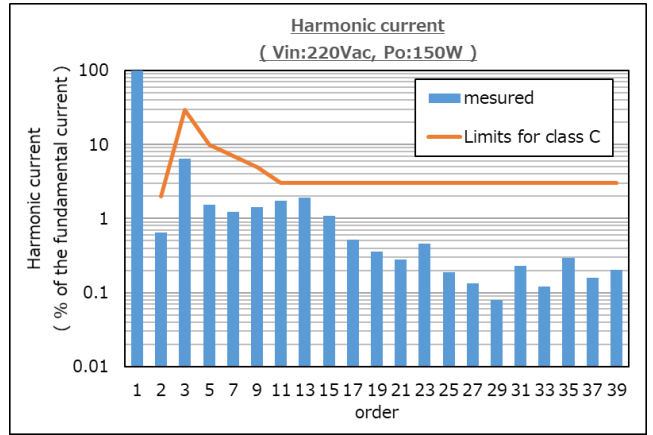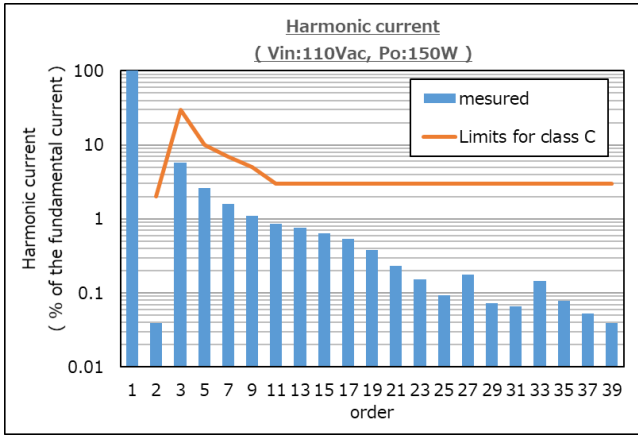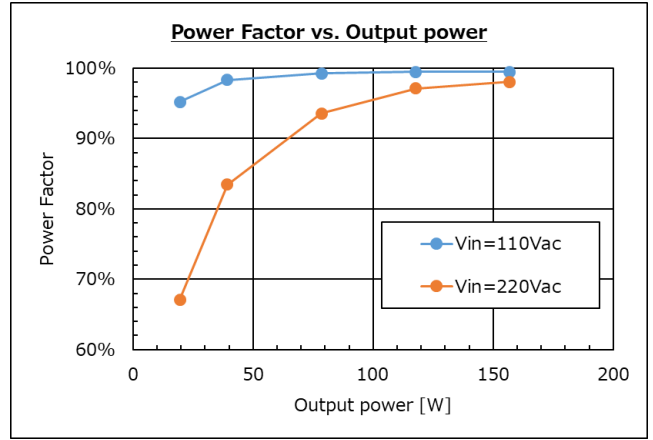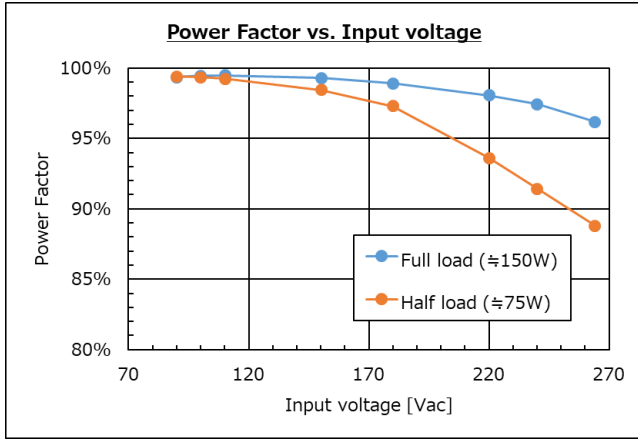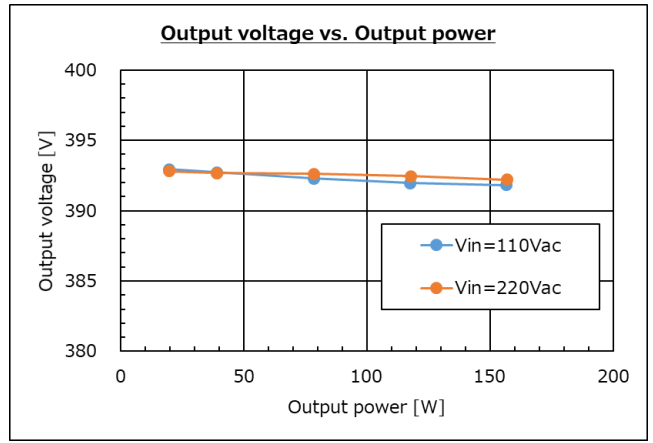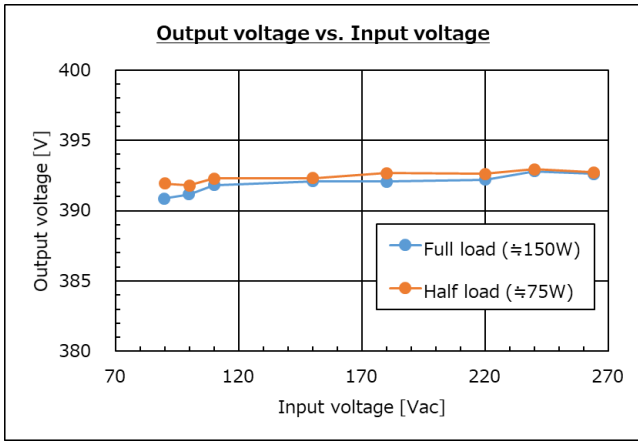

**7. Waveforms (AC input current)**

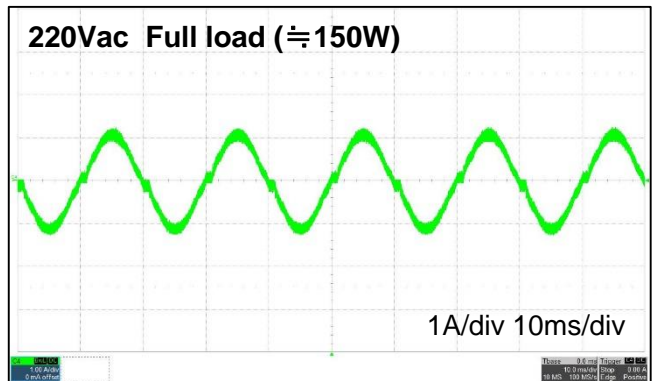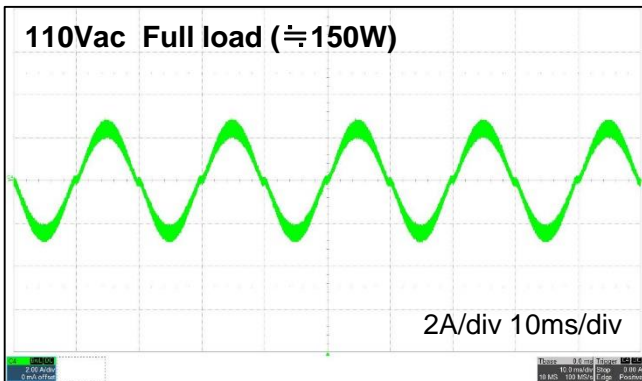


**8. Parts list**

| Component  | Item                     | Value      | Parts No.          | Maker  |
|------------|--------------------------|------------|--------------------|--------|
| C1,4       | Film capacitor           | 0.47u      | LE474-MX           | OKAYA  |
| C10        | Ceramic capacitor        | 470p       | DE2B3KY471KA3BM02F | MURATA |
| C101       | Ceramic capacitor        | 0.01u      |                    |        |
| C102,107   | Ceramic capacitor        | 0.1u       |                    |        |
| C103       | Ceramic capacitor        | 1u         |                    |        |
| C104       | Ceramic capacitor        | 1000p      |                    |        |
| C105       | Ceramic capacitor        | 2200p      |                    |        |
| C2,3       | Ceramic capacitor        | 2200p      | DE1E3KX222MN4AN01F | MURATA |
| C5         | Film capacitor           | 450V/1u    |                    |        |
| C7,8       | Electrolytic capacitor   | 450V/47u   |                    |        |
| C9         | Electrolytic capacitor   | 35V/22u    |                    |        |
| D1         | Bridge Diode             | 600V/10A   |                    |        |
| D2         | Diode                    | 600V/10A   | YG972S6R           | Fuji   |
| D3,6       | Diode                    | 200V/1A    |                    |        |
| F1         | Fuse                     | 250V/5A    |                    |        |
| IC101      | PFC IC                   |            | FA1B00N            | Fuji   |
| J1         | Connector                | 3pin       | B2P3-VH(LF)(SN)    | JST    |
| J2         | Connector                | 4pin       | B4P-VH(LF)(SN)     | JST    |
| J3         | Connector                | 2pin       | B2B-EH(LF)(SN)     | JST    |
| L1         | Inductor                 | 2A/12mH    |                    |        |
| L2         | Inductor                 | 300uH      |                    |        |
| Q1         | MOSFET                   | 600V/190mΩ | FMV60N190S2HF      | Fuji   |
| R1,2,3     | Resistor                 | 510k       |                    |        |
| R102       | Resistor                 | 2.7k       |                    |        |
| R103       | Resistor                 | 10k        |                    |        |
| R104       | Resistor                 | 51k        |                    |        |
| R105       | Resistor                 | 47         |                    |        |
| R106       | Resistor                 | 82k        |                    |        |
| R17        | Resistor                 | 100kΩ      |                    |        |
| R4         | Resistor                 | 10         |                    |        |
| R5         | Resistor                 | 100        |                    |        |
| R6,101     | Resistor                 | 47k        |                    |        |
| R7         | Resistor                 | 0.082      |                    |        |
| R8,9,10,11 | Resistor                 | 2MΩ        |                    |        |
| TH1        | Thermistor               | 3Ω         |                    |        |
| ZT1        | Transient/Surge Absorber | 470V       |                    |        |

**9. Inductor ( L2 )**

| Item       | Value    | Note                        |
|------------|----------|-----------------------------|
| Core size  | PQ 32/20 |                             |
| Inductance | 300μH    | 1,2 pin ~5,6 pin            |
| N1         | 28 turn  | start 1,2 pin : end 5,6 pin |
| N2         | 3 turn   | start 12 pin : end 11 pin   |

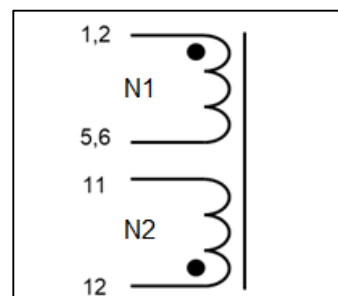**Wiring diagram**




### 10-3. RT pin

For the resistor of the RT pin, set the resistance greater than the on-width required for the circuit. Each parameter used in the calculation is as follows.

- ◆  $L_p$ : 300  $\mu\text{H}$  (typ.)
- ◆  $P_{out}$ : 150 W (target)
- ◆  $V_{ac(min)}$ : 90 Vrms
- ◆  $\eta$ : 0.9

※ $\eta$  is the input / output conversion efficiency of PFC, and the power factor is assumed as 1.

Calculate the input current (effective value).


$$150\text{W} \div 0.9 \div 90\text{Vrms} = 1.85\text{Arms}$$

The on-time is calculated by setting the peak value of the inductor current to twice the above input current.

$$300\mu\text{H} \times 2 \times 1.85\text{Arms} \times \sqrt{2} \div (90\text{Vrms} \times \sqrt{2}) = 12.3\mu\text{s}$$

From the calculation result, R5 is set to 51k $\Omega$ , because on-time is 13  $\mu\text{s}$ (typ.) when  $R_{rt}$  is 39k $\Omega$  on the data sheet. C7 is connected with a 1000 pF ceramic capacitor to prevent malfunction due to noise.

**RT pin circuit**

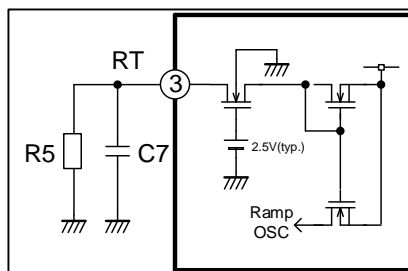

### 10-4. CS pin


The surge current due to drive current of MOSFET\_TR1 or the discharge current of the parasitic capacitance of the circuit flow through the current sensing resistor  $R_s$ . At the CS pin, connect a CR filter to prevent the OUT pin pulse from stopping due to false detection of these currents. After setting the cutoff frequency of the CR filter to be 1 to 2 MHz, check the actual operation and adjust.

- ◆  $R_4$ : 47  $\Omega$
- ◆  $C_6$ : 2200 pF

Calculate the cutoff frequency.

$$1 \div (2 \times \pi \times 47\Omega \times 2200\text{pF}) = 1.54\text{MHz}$$

**CS pin circuit**

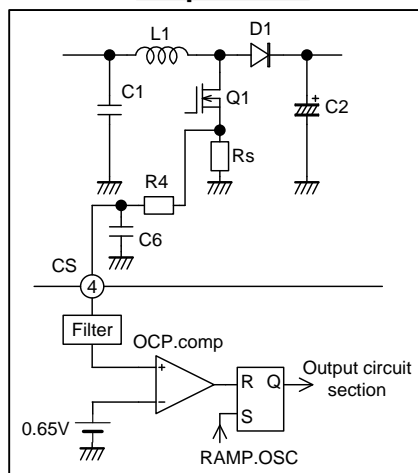


### 10-5. ZCD pin

The ZCD pin uses the auxiliary winding voltage to detect the timing when the transformer energy is reset. The recommended current value of the internal Zener diode at the ZCD pin is  $\pm 1.5\text{mA}$ . The current flowing through the Zener diode is limited by the resistor R6. The parameters used in the calculation are:

- ◆ N1: 28 turn
- ◆ N2: 3 turn
- ◆ Vac(max) : 264 Vrms
- ◆ Vout: 390 V
- ◆ Zd(+): 5.6 V (MIN.)
- ◆ Zd(-): -0.6 V (MAX.)

**ZCD pin circuit**

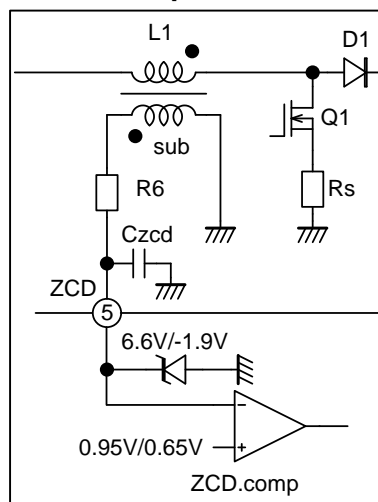

Calculate the ZCD pin voltage plus side.

$$(390\text{V} \times 3/28 - 5.6\text{V}) \div 1.5\text{mA} < R6$$

$$\underline{R6 > 24.1\text{k}\Omega}$$

Calculates the negative side of the ZCD pin voltage.

$$(-0.6\text{V} + \sqrt{2} \times 264\text{V} \times 3/28) \div 1.5\text{mA} < R6$$


$$\underline{R6 > 26.3\text{k}\Omega}$$

From the calculation results, R17 should be set to 26.1 k $\Omega$  or higher. In this reference design, 82 k $\Omega$  is selected in consideration of adjusting the resistance value of R6. When determining the resistance value, make adjustments while checking the MOSFET turn-on timing and ZCD pin waveform in the actual evaluation. The capacitor Czcd between the ZCD pin and the GND pin is not mounted.
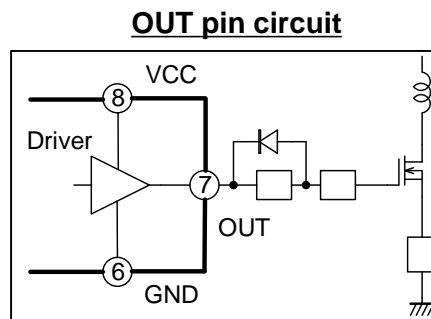
### 10-6. OUT pin

The OUT pin can directly drive the power MOSFET, but it must be used within the ratings of the source and sink current of the OUT pin. Make adjustments according to the circuit actually used and the power MOSFET. As a guide, set the lower limit of the resistance value. The parameters used in the calculation are:

- ◆ Vol: 1.2 V (typ.), Isink = 200 mA
- ◆ Voh: 10 V (MAX.), Isource = 50 mA
- ◆ Vcc: 12 V (measurement condition)
- ◆ VCC: 15 V (actual VCC pin voltage)
- ◆ Io: 1000 mA (sink)
- ◆ Io: 500 mA (source)



Calculate the internal resistance  $R_{sink}$  of the OUT pin when sinking the current.

$$R_{sink} = 1.2V \div 200mA = 6\Omega$$

Calculate the gate resistance  $R_g$  required when the power MOSFET is off.

$$15V \div (6\Omega + R_g) < 1000mA$$

$$R_g > 9\Omega$$

Calculate the internal resistance  $R_{source}$  of the OUT pin when sourcing current.

$$R_{source} = (12V - 10V) \div 50mA = 40\Omega$$


$$15V \div 40\Omega = 375mA$$

From the above calculation results, it was set as  $10\Omega$  for sink and  $10\Omega + 100\Omega$  for source. When the VCC voltage is 15 V, the output current  $I_o$  does not exceed 500 mA due to the voltage drop inside the IC, but when connecting to a MOSFET, be sure to connect a resistor. Determine the resistance value by adjusting the on / off timing in the actual evaluation. If the voltage fluctuation of the VCC pin is large, set the gate resistance at the maximum VCC voltage.

## 11. Reference board operating waveform
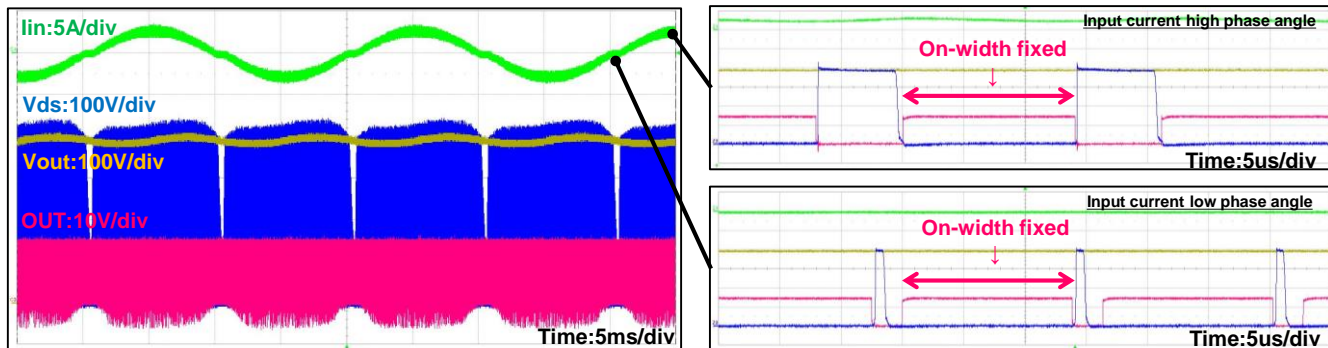
### 11-1. On-width fixed control

Fixed on-width control improves the power factor of the input current lin.




Vac: 90V / 50Hz, Po=150W, lin: input current, Vds: drain to source voltage, Vout: output voltage, OUT: voltage at OUT pin


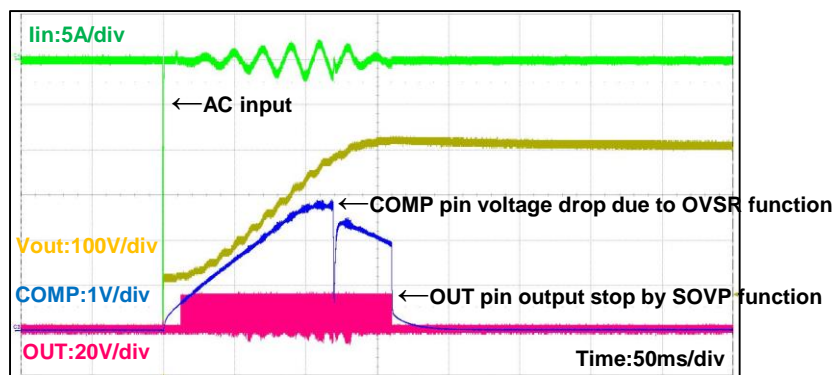
## 11-2. Overshoot reduction (OVSR) function


The overshoot reduction function suppresses the increase in COMP voltage at startup and narrows the on width, thereby reducing the output voltage overshoot at startup due to response delay. In addition, the overvoltage protection function built into the FB pin suppresses the rise in output voltage even after the overshoot reduction function operates.



Vac: 90V / 50Hz, Po=0W, lin: input current, Vout: output voltage, COMP: voltage at COMP pin, OUT: voltage at OUT pin
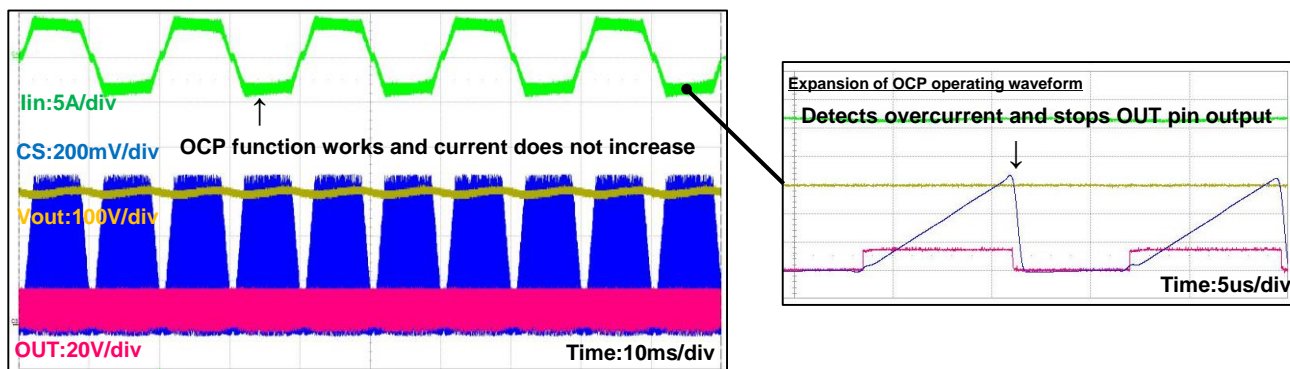
## 11-3. Overcurrent Protection (OCP) Function


The OCP function of the CS pin can suppress the peak current of the power MOSFET. When the CS pin voltage exceeds 0.65 V (typ.), the OUT pin output stops and the power MOSFET is turned off. This OCP function operates cycle by cycle of the OUT pin. Note that, this waveform is observed by increasing the current detection resistor in order to operate the OCP function.



Vac: 90V / 50Hz, lin: input current, Vout: output voltage, CS: voltage at CS pin, OUT: voltage at OUT pin
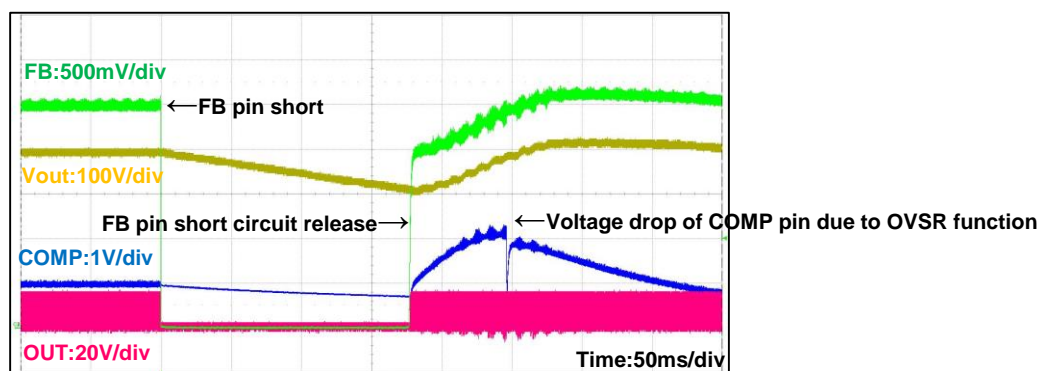
## 11-4. FB pin short circuit detection function

The FB pin has an FB pin short circuit detection function, and the OUT output is stopped when the FB pin voltage falls below 0.35V (typ.). When the FB pin short is released, the IC resumes operation and OUT output. The OVSR function also operates when the PFC circuit is turned on and off using the FB pin short-circuit detection circuit.



Vac: 90V / 50Hz, Po=20W, FB: voltage at FB pin, Vout: output voltage, COMP: voltage at COMP pin, OUT: voltage at OUT pin

## Notice

1. The contents of this note (Product Specification, Characteristics, Data, Materials, and Structure etc.) were prepared in Mar, 2021. The contents will subject to change without notice due to product specification change or some other reasons. In case of using the products stated in this document, the latest product specification shall be provided and the data shall be checked.
2. The application examples in this note show the typical examples of using Fuji products and this note shall neither assure to enforce the industrial property including some other rights nor grant the license.
3. Fuji Electric Co., Ltd. is always enhancing the product quality and reliability. However, semiconductor products may get out of order in a certain probability. Measures for ensuring safety, such as redundant design, spreading fire protection design, malfunction protection design shall be taken, so that Fuji Electric semiconductor product may not cause physical injury, property damage by fire and social damage as a result.
4. Products described in this note are manufactured and intended to be used in the following electronic devices and electric devices in which ordinary reliability is required:
  - Computer - OA equipment - Communication equipment (Pin) - Measuring equipment
  - Machine tool - Audio Visual equipment - Home appliance - Personal equipment
  - Industrial robot etc.
5. Customers who are going to use our products in the following high reliable equipments shall contact us surely and obtain our consent in advance. In case when our products are used in the following equipment, suitable measures for keeping safety such as a back-up-system for malfunction of the equipment shall be taken even if Fuji Electric semiconductor products break down:
  - Transportation equipment (in-vehicle, in-ship etc.) - Communication equipment for trunk line
  - Traffic signal equipment - Gas leak detector and gas shutoff equipment
  - Disaster prevention/Security equipment - Various equipment for the safety.
6. Products described in this note shall not be used in the following equipments that require extremely high reliability:
  - Space equipment - Aircraft equipment - Atomic energy control equipment
  - Undersea communication equipment - Medical equipment.
7. When reprinting or copying all or a part of this note, our company's acceptance in writing shall be obtained.
8. If obscure parts are found in the contents of this note, contact Fuji Electric Co., Ltd. or a sales agent before using our products. Fuji Electric Co., Ltd. and its sales agents shall not be liable for any damage that is caused by a customer who does not follow the instructions in this cautionary statement.

- The contents will subject to change without notice due to product specification change etc.
  - Application examples and component in this sheet is for the purpose of assisting in the design. Therefore, This sheet has not been made in consideration of the margin.
  - Before using, Please design in consideration of the parts variation and use condition.