

---

---

# Chapter 5

## Protection Circuit Design

---

---

CONTENTS		Page
1	Short circuit (overcurrent) protection .....	5-2
2	Overvoltage protection .....	5-6

This section explains the protection circuit design.

---

---

## 1 Short circuit (overcurrent) protection

### 1-1 Short circuit withstand capability

In the event of a short circuit, first the IGBT's collector current will rise, once it has reached a certain level, the C-E voltage will spike. Depending on the device's characteristics, during the short-circuit, the collector current can be kept at or below a certain level, however the IGBT will still continue to be subjected to a heavy load, that is, high voltage and high current. Therefore, this condition must be removed as soon as possible.

However, the amount of time allowed between the start of a short circuit until the current is cut off, is limited by the IGBT's short circuit withstand capability, which is determined by the amount of time, as illustrated in Fig. 5-1. The IGBT's short circuit withstand capability is defined as the start of the short-circuit current until the module is destroyed. Therefore, when the IGBT is short-circuited, large current is need to be cut off within the short circuit withstand capability.

The withstand capability depends on collector to emitter voltage  $V_{CE}$ , gate to emitter voltage  $V_{GE}$  and/or junction temperature  $T_j$ .

In general, the larger supply voltage and/or the higher junction temperature are, the lower the withstand capability will be.

For more information on withstand capability, referred to the application manual or technical data.

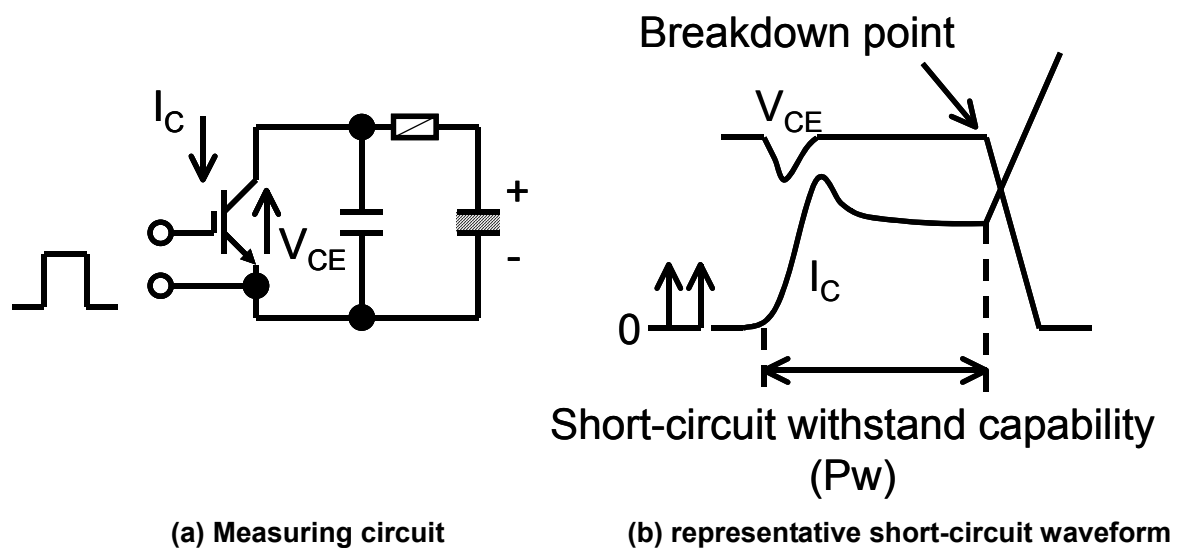
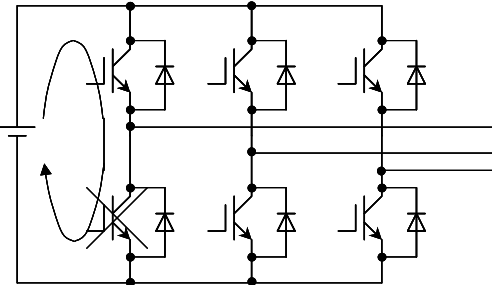
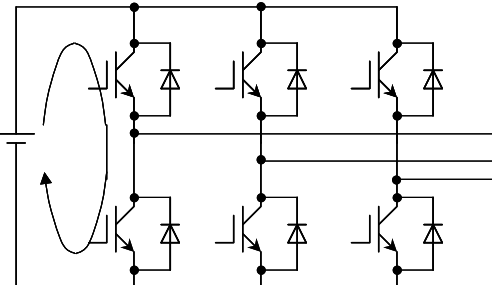
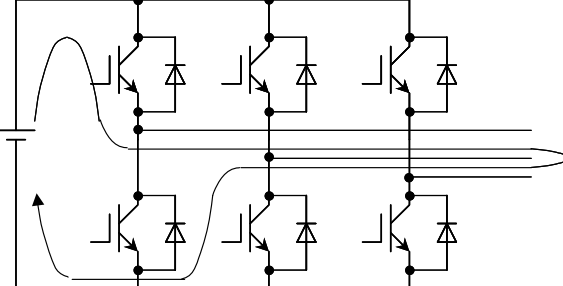
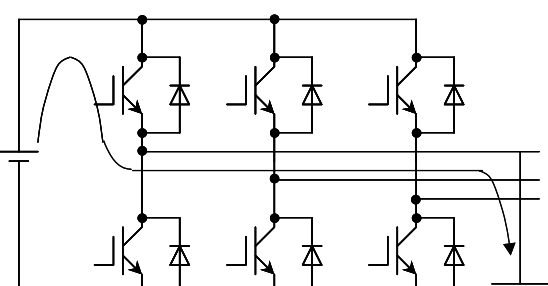


Fig. 5-1 Measuring circuit and waveform

1-2 Short-circuit modes and causes

Table 5-1 lists the short-circuit modes and causes that occur in inverters.

Table 5-1 Short circuit mode and cause

Short circuit mode	Cause
<p>Arm short circuit</p> 	<p>Transistor or diode destruction</p>
<p>Series arm short circuit</p> 	<p>Faulty control/drive circuit or noise induce malfunction</p>
<p>Short in output circuit</p> 	<p>Miss wiring or dielectric breakdown of load</p>
<p>Ground fault</p> 	<p>Miss wiring or dielectric breakdown of load</p>

### 1-3 Short-circuit (overcurrent) detection

#### 1) Detection in the circuit

As described previously, in the event of a short-circuit, the IGBT must be protected as soon as possible. Therefore, the time from overcurrent detection to the complete turn-off in each circuit must work effectively as fast as possible.

Since the IGBT turns off very quickly, if the overcurrent is shut off using an ordinary drive signal, the collector-emitter voltage will rise due to the back-emf from parasitic inductances, and then the IGBT would have chance to be destroyed by overvoltage (RBSOA destructions). Therefore, it is recommended that when shutting off the overcurrent that the IGBT be turned off gently (Soft turn-off).

Figure 5-2 shows the insertion methods for overcurrent detectors, and Table 5-2 lists the features of the various methods along with their detection possibilities. After determining what kind of protection is necessary, select the most appropriate form of detection.

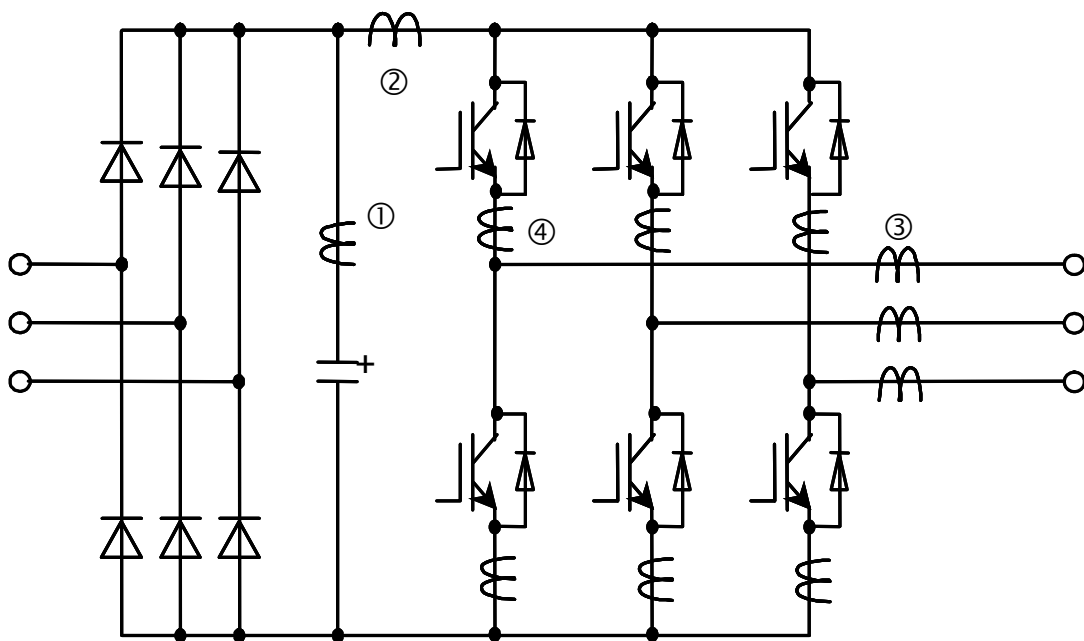


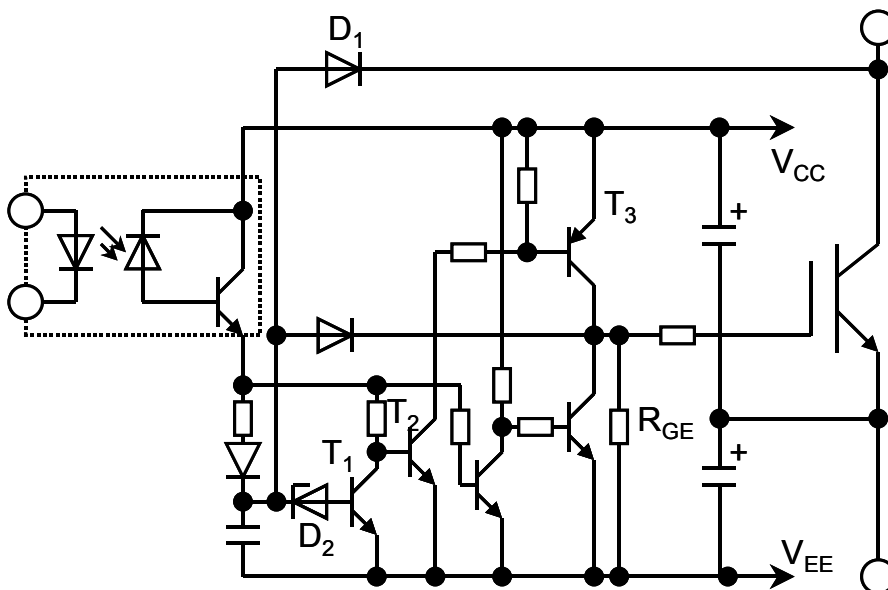
Fig. 5-2 Overcurrent detector insertion methods

Table 5-2 Overcurrent detector insertion positions and function


Detector insertion position	Features	Detection function
Insertion in line with smoothing capacitor Fig.5-2/①	<ul style="list-style-type: none"> <li>• AC current transformer available</li> <li>• Low detection precision</li> </ul>	<ul style="list-style-type: none"> <li>• Arm short-circuit</li> <li>• Short in output circuit</li> <li>• Series arm short-circuit</li> <li>• Ground fault</li> </ul>
Insertion at inverter input Fig.5-2/②	<ul style="list-style-type: none"> <li>• Necessary to use DC current transformer</li> <li>• Low detection precision</li> </ul>	<ul style="list-style-type: none"> <li>• Arm short-circuit</li> <li>• Short in output circuit</li> <li>• Series arm short-circuit</li> <li>• Ground fault</li> </ul>
Insertion at inverter output Fig.5-2/③	<ul style="list-style-type: none"> <li>• AC current transformer available for high frequency output equipment</li> <li>• High detection precision</li> </ul>	<ul style="list-style-type: none"> <li>• Short in output circuit</li> <li>• Ground fault</li> </ul>
Insertion in line with switches Fig.5-2/④	<ul style="list-style-type: none"> <li>• Necessary to use DC current transformer</li> <li>• High detection precision</li> </ul>	<ul style="list-style-type: none"> <li>• Arm short-circuit</li> <li>• Short in output circuit</li> <li>• Series arm short-circuit</li> <li>• Ground fault</li> </ul>

## 2) Detecting using $V_{CE(sat)}$

This method has a feature of protection against all possible short-circuit types listed in Table5-1. Since all operations from overcurrent detection to protection are done on the drive circuit side, the fastest protection is possible. A short-circuit protection schematic, based in  $V_{CE(sat)}$  detection, is shown in Fig.5-3.

Fig. 5-3 Short-circuit protection schematic based in  $V_{CE(sat)}$  detection

This circuit uses  $D_1$  to constantly monitor the collector-emitter voltage, so if during operation the IGBT's collector-emitter voltage rises above the limit at  $D_2$ , then a short-circuit condition will be detected and  $T_1$  will be switched on while  $T_2$  and  $T_3$  are switched off. At this time, the accumulated charge at the gate is slowly released through the  $R_{GE}$ , so a large voltage spike is prevented when the IGBT is turned off. Gate driver hybrid IC<sub>S</sub> (model VLA517) have similar kind of protective circuit built in, thereby simplifying the drive circuit design. For more details, refer to Chapter 7 "Drive Circuit Design". Fig. 5-4 shows an example of IGBT waveforms in short circuit protection.

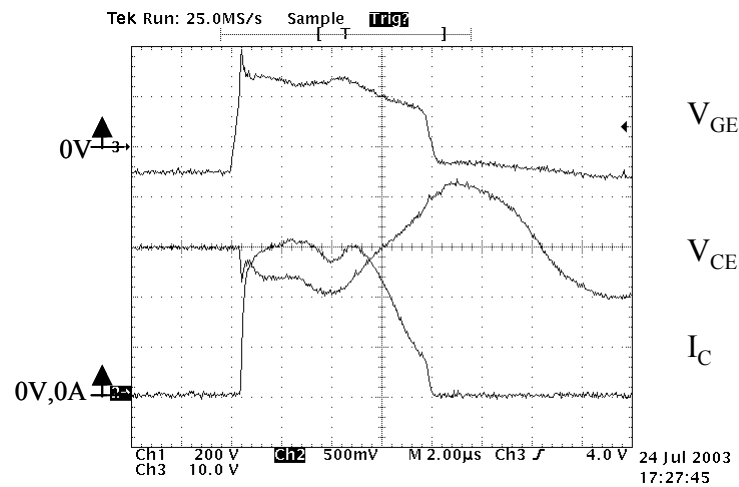

2MBI300UD-120

$E_d=600\text{V}$ ,  $V_{GE}=+15\text{V}$ ,  $-5\text{V}$  (VLA517),  $R_G=3.3\Omega$ ,  $T_j=125^\circ\text{C}$

$V_{CE}=200\text{V/div}$ ,  $I_C=250\text{A}$ ,  $V_{GE}=10\text{V/div}$ ,  $t=2\mu\text{s/div}$

**Fig. 5-4 Waveforms during short circuit protection**


## 2 Overvoltage protection

### 2.1 Overvoltage causes and their suppression
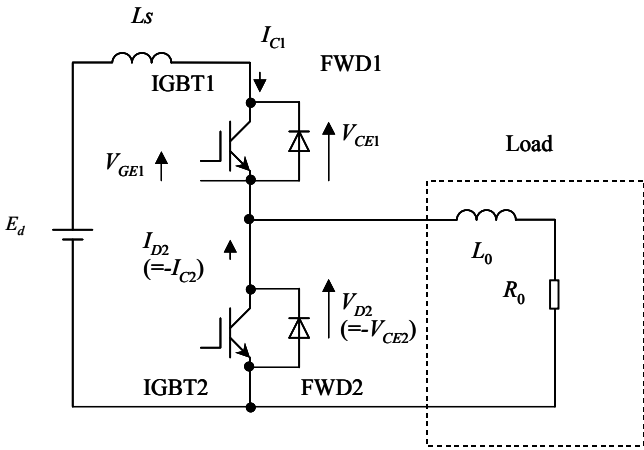
#### 1) Overvoltage causes

Due to the fast switching feature of IGBTs at turn-off and/or during FWD reverse recovery, the instantaneous rate in current over time ( $di/dt$ ) would have very high value. Therefore the parasitic inductances to the module would produce a high turn-off surge voltage ( $V=L(di/dt)$ ).

In this section, an example of solutions both for IGBT and FWD are described with explanation of the root causes and practical methods to suppress the surge voltage with typical IGBT waveforms at turn-off. To demonstrate the turn-off surge voltage, a simplified chopper circuit and the IGBT turn-off voltage and current waveforms are shown in Fig. 5-5 and 5-6, respectively.



Ed: DC supply voltage, Ls: Main circuit parasitic inductance, Load:L0,R0

Fig. 5-5 Chopper circuit

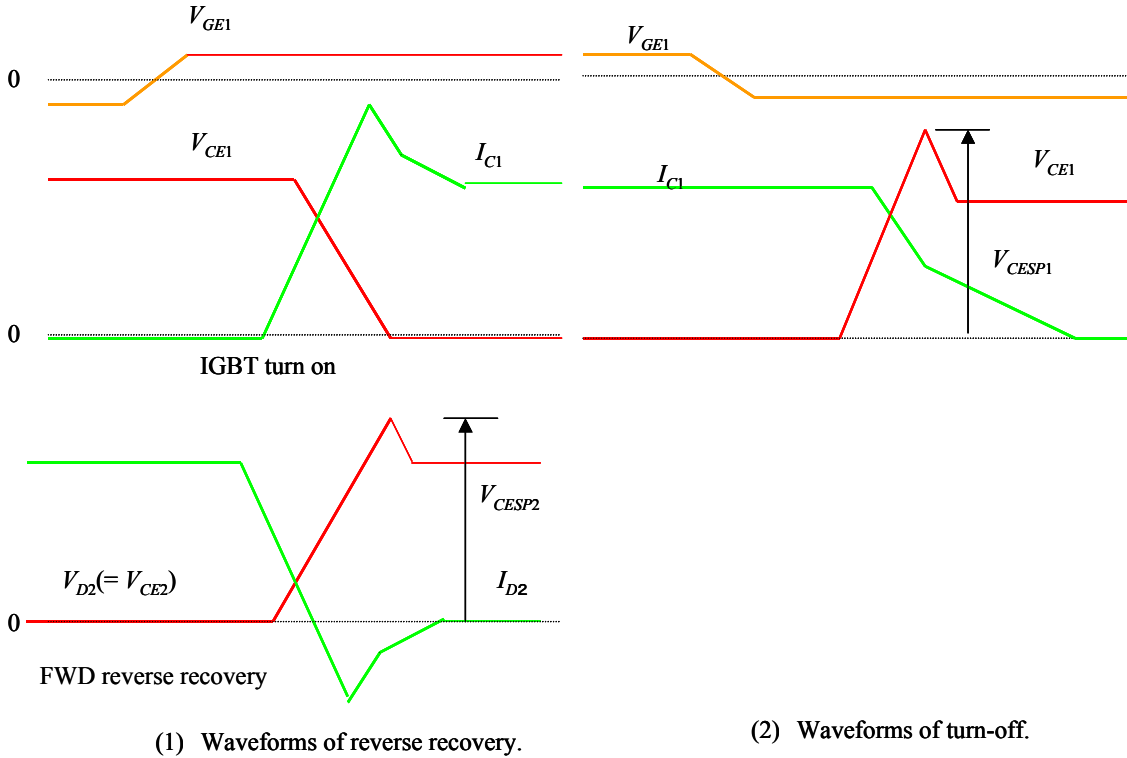


Fig. 5-6 Switching waveforms

The turn-off surge voltage peak  $V_{CESP}$  can be calculated as follows:

$$V_{CESP} = Ed + (-L_s \cdot dI_C / dt) \dots\dots\dots \textcircled{1}$$

dIc/dt: Instantaneous rate in current over time

If  $V_{CESP}$  exceeds the maximum C-E ( $V_{CES}$ ) rating of IGBT, IGBT module would be destroyed.

## 2) Overvoltage suppression methods

Several methods for suppressing the turn-off surge voltage, the cause for overvoltage, are listed below:

- a. Control the surge voltage with an additional protection circuit (snubber circuit) to the IGBT.  
A film capacitor in the snubber circuit, which is connected as close as possible to the IGBT, works to bypass the high frequency surge currents.
- b. Adjust the IGBT drive circuit's  $-V_{GE}$  and/or  $R_G$  in order to reduce the  $di/dt$  value. (Refer to Chapter 7, "Drive Circuit Design".)
- c. Place the electrolytic capacitor as close as possible to the IGBT in order to reduce the parasitic inductance of the wiring. A low impedance capacitors have better effect.
- d. To reduce the inductance of the main circuit as well as the snubber circuit parasitic inductances, thicker and shorter connections are recommended. Laminated bus bars are best solution to reduce parasitic inductances.

## 2.2 Types of snubber circuits and their features

Snubber circuits can be classified into two types: individual and lump. Individual snubber circuits are connected to each IGBT, while lump snubber circuits are connected between the DC power-supply bus and the ground for centralized protection.

### 1) Individual snubber circuits

Examples of typical individual snubber circuits are listed below.

- a) RC snubber circuit
- b) Charge and discharge RCD snubber circuit
- c) Discharge-suppressing RCD snubber circuit

Table 5-3 shows the schematic of each type of individual snubber circuit, its features, and an outline of its main applications.

### 2) Lump snubber circuits

Examples of typical snubber circuits are listed below.



- a) C snubber circuits
- b) RCD snubber circuits


Lump snubber circuits are becoming increasingly popular due to circuit simplification.

Table 5-4 shows the schematic of each type of lump snubber circuit, its features, and an outline of its main applications. Table 5-5 shows the capacity selection of a C type snubber circuit. Fig. 5-7 shows the current and voltage turn-off waveforms for an IGBT connected to a lump snubber circuit.



Table 5-3 Individual snubber circuits

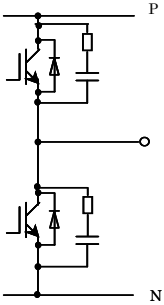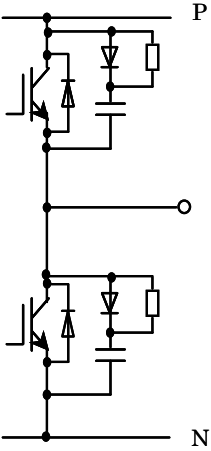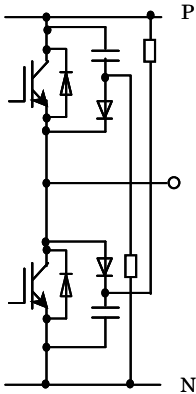Snubber circuit schematic	Circuit features (comments)	Main application
<p>RC snubber circuit</p> 	<ul style="list-style-type: none"> <li>• Very effective on turn-off surge voltage suppression</li> <li>• Best for chopper circuits</li> <li>• For high power IGBTs, the low resistance snubber resistance is necessary, which results in increase in turn-off collector current and higher IGBT load.</li> </ul>	<p>Welding</p> <p>Switching power supply</p>
<p>Charge and discharge RCD snubber circuit</p> 	<ul style="list-style-type: none"> <li>• The moderate effect in turn-off surge voltage suppression.</li> <li>• In contrast to the RC snubber circuit, additional snubber diodes connected parallel to the snubber resistance.. This diode enable not to use low snubber resistance. consequently preventing the IGBT higher load turn-on issue in RC snubber solution above.</li> <li>• Since the power dissipation of the snubber circuit (primarily caused by the snubber resistance) is much higher than that of a discharge suppressing snubber circuit below, it is not considered suitable for high frequency switching applications.</li> <li>• The power dissipation caused by the resistance of this circuit can be calculated as follows:</li> </ul> $P = \frac{L \cdot I_o^2 \cdot f}{2} + \frac{C_s \cdot E_d^2 \cdot f}{2}$ <p>L: Parasitic inductance of main circuit,  <i>I</i><sub>o</sub>: Collector current at IGBT turn-off,  <i>C</i><sub>s</sub>: Capacitance of snubber capacitor,  <i>E</i><sub>d</sub>: DC supply voltage,  <i>f</i>: Switching frequency</p>	

<p>Discharge suppressing RCD snubber circuit</p> 	<ul style="list-style-type: none"> <li>• Limited effect on turn-off surge voltage suppression</li> <li>• Suitable for high-frequency switching</li> <li>• Small power dissipation of snubber circuit i.</li> <li>• The power dissipation caused by the resistance of this circuit can be calculated as follows:</li> </ul> $P = \frac{L \cdot I_o^2 \cdot f}{2}$ <p>L: Parasitic inductance of main circuit  <i>I</i><sub>o</sub>: Collector current at IGBT turn-off                  f :Switching frequency</p>	<p>Inverter</p>
--	---	-----------------

**Table 5-4 Lump snubber circuits**

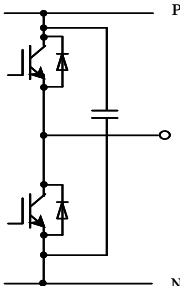
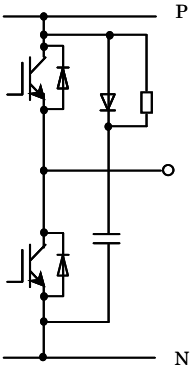
Snubber circuit schematic	Circuit features (comments)	Main application
<p>C snubber circuit</p> 	<ul style="list-style-type: none"> <li>• The simplest topology.</li> <li>• The LC resonance circuit, which consists of a main circuit parasitic inductance and snubber capacitor, may have a chance of the C-E voltage oscillation.</li> </ul>	<p>Inverter</p>
<p>RCD snubber circuit</p> 	<ul style="list-style-type: none"> <li>• In case inappropriate snubber diode is used, a high spike voltage and/or the output voltage oscillation in the diodes reverse recovery would be observed</li> </ul>	<p>Inverter</p>

Table 5-5 Guidelines for designing the lump C snubber circuit capacitance

Module rating	Item	Drive conditions <sup>*1</sup>		Main circuit wiring inductance ( $\mu\text{H}$ )	Snubber capacitance $C_s$ ( $\mu\text{F}$ )
		$-V_{\text{GE}}$ (V)	$R_G$ ( $\Omega$ )		
600V	50A	max 15V	min.43 $\Omega$	-	0.47 $\mu\text{F}$
	75A		min.30 $\Omega$		
	100A		min.13 $\Omega$		
	150A		min.9 $\Omega$	max 0.20 $\mu\text{H}$	1.5 $\mu\text{F}$
	200A		min.6.8 $\Omega$ .	max.0.16 $\mu\text{H}$	2.2 $\mu\text{F}$
	300A		min.4.7 $\Omega$	max.0.10 $\mu\text{H}$ .	3.3 $\mu\text{F}$
	400A		min.6.0 $\Omega$	max.0.08 $\mu\text{H}$ .	4.7 $\mu\text{F}$
1200V	50A	max 15V	min.22 $\Omega$	-	0.47 $\mu\text{F}$
	75A		min.4.7 $\Omega$		
	100A		min.2.8 $\Omega$		
	150A		min.2.4 $\Omega$	max.0.20 $\mu\text{H}$ .	1.5 $\mu\text{F}$
	200A		min.1.4 $\Omega$	max.0.16 $\mu\text{H}$ .	2.2 $\mu\text{F}$
	300A		min.0.93 $\Omega$	max.0.10 $\mu\text{H}$ .	3.3 $\mu\text{F}$

\*1: Typical external gate resistance of V series IGBT are shown.

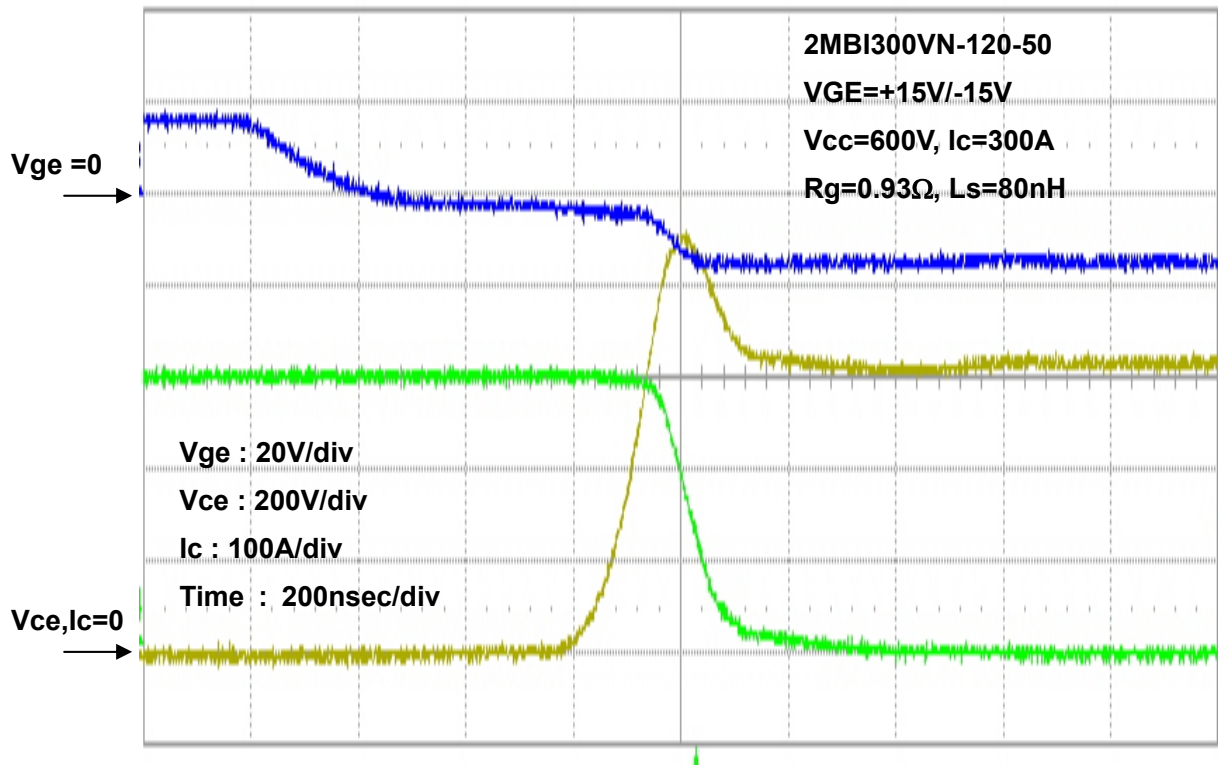


Fig. 5-7 Current and voltage waveforms of IGBT with lump snubber circuit at turn-off

### 2-3 Discharge-suppressing RCD snubber circuit design

The discharge suppressing RCD can be considered the most suitable snubber circuit for IGBTs. Basic design methods for this type of circuit are explained in the following.

#### 1) Study of applicability

Figure 5-8 is the turn-off locus waveform of an IGBT in a discharge-suppressing RCD snubber circuit. Fig. 5-9 shows the IGBT current and voltage waveforms at turn-off.

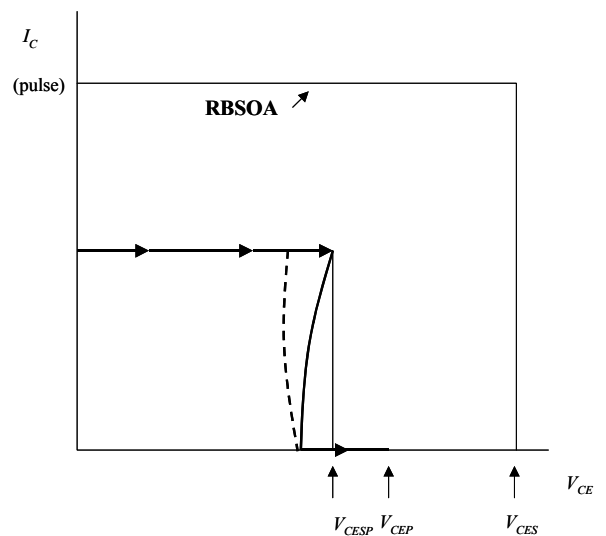


Fig. 5-8 Turn-off locus waveform of IGBT

The discharge-suppressing RCD snubber circuit is activated when the IGBT C-E voltage starts to exceed the DC supply voltage. The dotted line in diagram Fig. 5-8 shows the ideal operating locus of an IGBT. In an actual application, the wiring inductance of the snubber circuit or a transient forward voltage drop in the snubber diode can cause a spike voltage at IGBT turn-off. This spike voltage causes the sharp-cornered locus indicated by the solid line in Fig. 5-8.

The discharge-suppressing RCD snubber circuits applicability is decided by whether or not the IGBTs operating locus is within the RBSOA at turn-off.

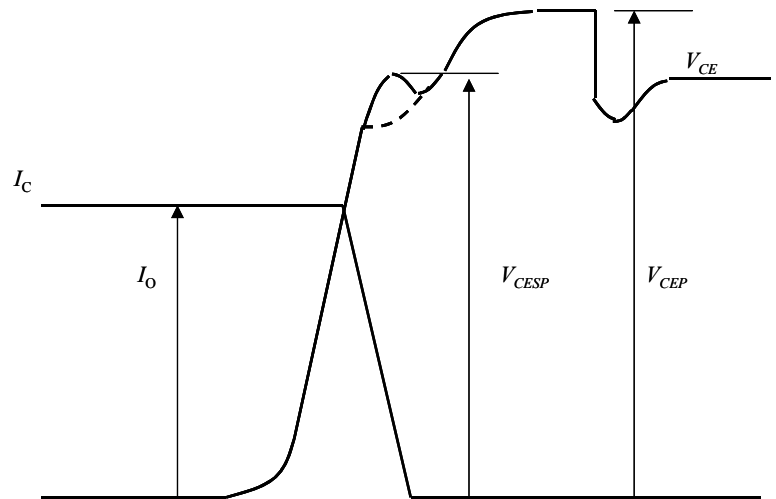


Fig. 5-9 Voltage and current waveforms at turn-off

The spike voltage at IGBT turn-off is calculated as follows:

$$V_{CESP} = Ed + V_{FM} + (-L_s \bullet dIc / dt) \dots\dots\dots ②$$

Ed: Dc supply voltage

V<sub>FM</sub>: Transient forward voltage drop in snubber diode

The reference values for the transient forward voltage drop in snubber diodes is as follows:

600V class: 20 to 30V

1200V class: 40 to 60V

L<sub>s</sub>: Snubber circuit wiring parasitic inductance

dIc/dt: The instantaneous rate in collector current over time in IGBT turn-off

## 2) Calculating the capacitance of the snubber capacitor (Cs)

The minimum capacitance of a snubber capacitor is calculated as follows:

$$C_s = \frac{L \bullet I_o^2}{(V_{CEP} - Ed)^2} \dots\dots\dots ③$$

L: Main circuit wiring parasitic inductance

I<sub>o</sub>: Collector current at IGBT turn-off

V<sub>CEP</sub>: Snubber capacitor peak voltage

Ed: DC supply voltage

V<sub>CEP</sub> must be lower than IGBT C-E breakdown voltage. High frequency capacitors such as film capacitors are recommended.

### 3) Calculating Snubber resistance (Rs)

The function required of snubber resistance is to discharge the electric charge accumulated in the snubber capacitor before the next IGBT turn-off event.

To discharge 90% of the accumulated energy by the next IGBT turn-off event, the snubber resistance must be as follows:

$$R_s \leq \frac{1}{2.3 \cdot C_s \cdot f} \dots\dots\dots ④$$

f: Switching frequency

If the snubber resistance is set too low, the snubber circuit current will oscillate and the peak collector current at the IGBT turn-off will increase. Therefore, set the snubber resistance in a range below the value calculated in the equation.

Independently to the resistance, the power dissipation loss P (Rs) is calculated as follows:

$$P(R_s) = \frac{L \cdot I_o^2 \cdot f}{2} \dots\dots\dots ⑤$$

### 4) Snubber diode selection

A transient forward voltage drop in the snubber diode is one factor that would cause a spike voltage at IGBT turn-off.

If the reverse recovery time of the snubber diode is too long, then the power dissipation loss will also be much greater during high frequency switching. If the snubber diode's reverse recovery is too hard, then the IGBT C-E voltage will drastically oscillate.

Select a snubber diode that has a low transient forward voltage, short reverse recovery time and a soft recovery.

### 5) Snubber circuit wiring precautions

The snubber circuit's wiring inductance is one of the main causes of spike voltage, therefore it is important to design the circuit with the lowest inductance possible.

## 2-4 Example of characteristic of spike voltage

The spike voltage shows various behaviors depending on the operation, drive and circuit conditions. Generally, the spike voltage becomes higher when the collector voltage is higher, the circuit inductance is larger, and the collector current is larger. As an example of spike voltage characteristic, the current dependence of spike voltage at IGBT turn-off and FWD reverse recovery is shown in Figure 5-10.

As this figure shows, the spike voltage at IGBT turn-off becomes higher when the collector current is higher, but the spike voltage at FWD reverse recovery becomes higher when the current is low. Generally, the spike voltage during reverse recovery becomes higher when the collector current is in the low current area that is a fraction of the rated current.

The spike voltage shows various behaviors depending on the operation, drive and circuit conditions. Therefore, make sure that the current and voltage can be kept within the RBSOA described in the specification in any expected operating condition of the system.

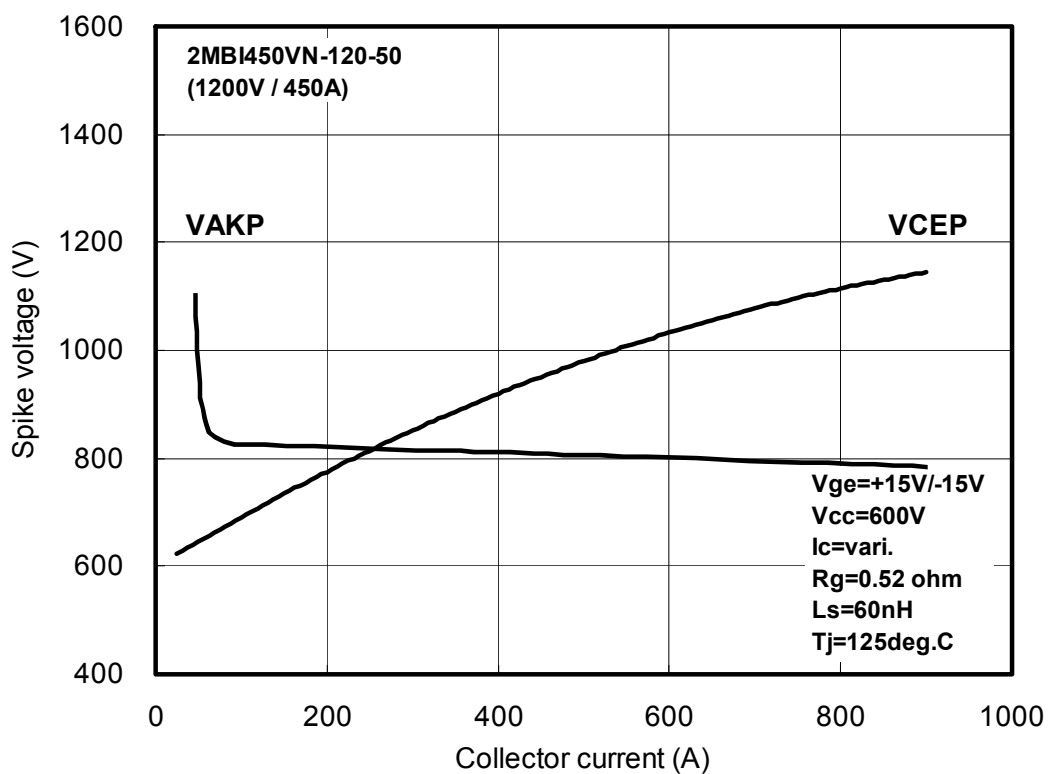


Fig. 5-10 Spike voltages dependency on collector current

## 2-5 Spike voltage suppression circuit - clamp circuit -

In general, spike voltage generated between collector to emitter can be suppressed by means of decreasing the stray inductance or installing snubber circuit. However, it may be difficult to decrease the spike voltage under the hard operating conditions.

For this case, it is effective to install the active clamp circuits, which is one of the spike voltage suppressing circuits.

Fig. 5-11 shows the example of active clamp circuits.

In the circuits, Zener diode and a diode connected with the anti-series in the Zener diode are added.

When the  $V_{ce}$  over breakdown voltage of Zener diode is applied, IGBT will be turned-off with the similar voltage as breakdown voltage of Zener diode. Therefore, installing the active clamp circuits can suppress the spike voltage.

Moreover, avalanche current generated by breakdown of Zener diode, charge the gate capacitance so as to turn-on the IGBT. As the result,  $di/dt$  at turn-off become lower than that before adding the clamp circuit (Refer to Fig. 5-12). Therefore, because switching loss may be increased, apply the clamp circuit after various confirmations for design of the equipment.

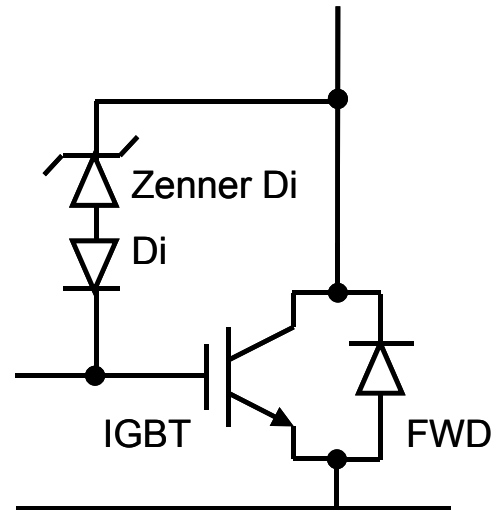


Fig. 5-11 Active clamp circuit

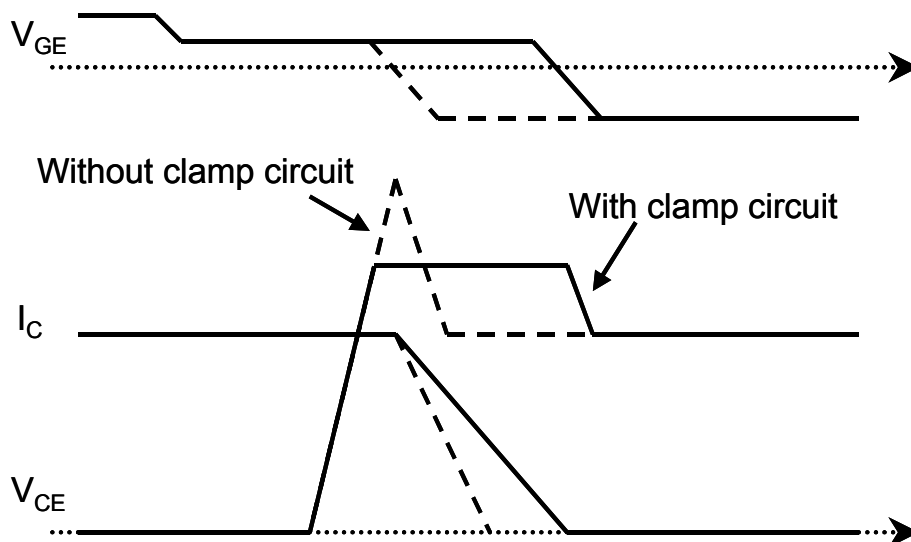


Fig. 5-12 Schematic waveform for active clamp circuit



## WARNING

1. This Catalog contains the product specifications, characteristics, data, materials, and structures as of May 2011.  
The contents are subject to change without notice for specification changes or other reasons. When using a product listed in this Catalog, be sure to obtain the latest specifications.
2. All applications described in this Catalog exemplify the use of Fuji's products for your reference only. No right or license, either express or implied, under any patent, copyright, trade secret or other intellectual property right owned by Fuji Electric Co., Ltd. is (or shall be deemed) granted. Fuji Electric Co., Ltd. makes no representation or warranty, whether express or implied, relating to the infringement or alleged infringement of other's intellectual property rights which may arise from the use of the applications described herein.
3. Although Fuji Electric Co., Ltd. is enhancing product quality and reliability, a small percentage of semiconductor products may become faulty. When using Fuji Electric semiconductor products in your equipment, you are requested to take adequate safety measures to prevent the equipment from causing a physical injury, fire, or other problem if any of the products become faulty. It is recommended to make your design failsafe, flame retardant, and free of malfunction.
4. The products introduced in this Catalog are intended for use in the following electronic and electrical equipment which has normal reliability requirements.
  - Computers
  - OA equipment
  - Communications equipment (terminal devices)
  - Measurement equipment
  - Machine tools
  - Audiovisual equipment
  - Electrical home appliances
  - Personal equipment
  - Industrial robots etc.
5. If you need to use a product in this Catalog for equipment requiring higher reliability than normal, such as for the equipment listed below, it is imperative to contact Fuji Electric Co., Ltd. to obtain prior approval. When using these products for such equipment, take adequate measures such as a backup system to prevent the equipment from malfunctioning even if a Fuji's product incorporated in the equipment becomes faulty.
  - Transportation equipment (mounted on cars and ships)
  - Trunk communications equipment
  - Traffic-signal control equipment
  - Gas leakage detectors with an auto-shut-off feature
  - Emergency equipment for responding to disasters and anti-burglary devices
  - Safety devices
  - Medical equipment
6. Do not use products in this Catalog for the equipment requiring strict reliability such as the following and equivalents to strategic equipment (without limitation).
  - Space equipment
  - Aeronautic equipment
  - Nuclear control equipment
  - Submarine repeater equipment
7. Copyright ©1996-2011 by Fuji Electric Co., Ltd. All rights reserved.  
No part of this Catalog may be reproduced in any form or by any means without the express permission of Fuji Electric Co., Ltd.
8. If you have any question about any portion in this Catalog, ask Fuji Electric Co., Ltd. or its sales agents before using the product. Neither Fuji Electric Co., Ltd. nor its agents shall be liable for any injury caused by any use of the products not in accordance with instructions set forth herein.