

Fuji 7<sup>th</sup> Generation IGBT Module  
X Series  
Chapter 2  
Precaution for Use



**Application Manual**

## Warning:

This manual contains the product specifications, characteristics, data, materials, and structures as of June 2021.

The contents are subject to change without notice for specification changes or other reasons. When using a product listed in this manual, be sure to obtain the latest specifications.

All applications described in this manual exemplify the use of Fuji's products for your reference only. No right or license, either express or implied, under any patent, copyright, trade secret or other intellectual property right owned by Fuji Electric Co., Ltd. is (or shall be deemed) granted. Fuji Electric Co., Ltd. makes no representation or warranty, whether express or implied, relating to the infringement or alleged infringement of other's intellectual property rights which may arise from the use of the applications described herein.

## Cautions

### (1) During transportation and storage

Keep locating the shipping carton boxes to suitable side up. Otherwise, unexpected stress might affect to the boxes. For example, bend the terminal pins, deform the inner resin case, and so on.

When you throw or drop the product, it gives the product damage.

If the product is wet with water, that it may be broken or malfunctions, please subjected to sufficient measures to rain or condensation.

Temperature and humidity of an environment during transportation are described in the specification sheet. There conditions shall be kept under the specification.

### (2) Assembly environment

Since this power module device is very weak against electro static discharge, the ESD countermeasure in the assembly environment shall be suitable within the specification described in specification sheet. Especially, when the conducting pad is removed from control pins, the product is most likely to get electrical damage.

### (3) Operating environment

If the product had been used in the environment with acid, organic matter, and corrosive gas (hydrogen sulfide, sulfurous acid gas), the product's performance and appearance can not be ensured easily.

## Chapter 2 Precaution for Use

1. Maximum Junction Temperature $T_{vj}$ , $T_{vjop}$	2-2
2. Short-Circuit (Overcurrent) Protection	2-2
3. Overvoltage Protection and Safe Operating Area	2-3
4. Parallel Connection	2-9
5. Mounting Instruction	2-10

The 7<sup>th</sup> generation X-series IGBT modules contains the same Field Stop (FS) and trench gate structure that had been introduced for the 5<sup>th</sup> generation U-series and 6<sup>th</sup> generation V-series, respectively. Beside that the overall characteristics have been improved by thinning the wafer thickness and optimizing the trench structure.

This chapter explains how to use the 7<sup>th</sup> generation X-series IGBT modules.

## 1. Maximum Junction Temperature $T_{vj}$ , $T_{vjop}$

The characteristics of the 7<sup>th</sup> generation X-series modules have been improved to provide a continuous operation junction temperature  $T_{vjop}$  of maximum 175°C. Operating conditions must never be defined to exceed the maximum junction temperature. Please be aware using these products beyond the maximum temperature may result in a reduction of the product life time, such as power cycle endurance.

## 2. Short-Circuit (Overcurrent) Protection

If a short-circuit occurs, the IGBT collector current  $I_C$  will increase. If  $I_C$  reaches a saturated value, the voltage between collector and emitter ( $V_{CE}$ ) will rapidly increase. Because of this behavior the collector current during short circuit is suppressed to a certain level. The short circuit condition has to be removed immediately as high voltage and high current is applied to the IGBT at the same time.

Fig. 2-1 shows the relation between the applied voltage  $V_{CC}$  and the short-circuit withstand capability (short circuit time) for the 650V and 1200V X-series modules. Please define the short circuit detection time and protection intervention time in order to not exceed the withstand capability. This has to be applied according to the operating requirements of the application.

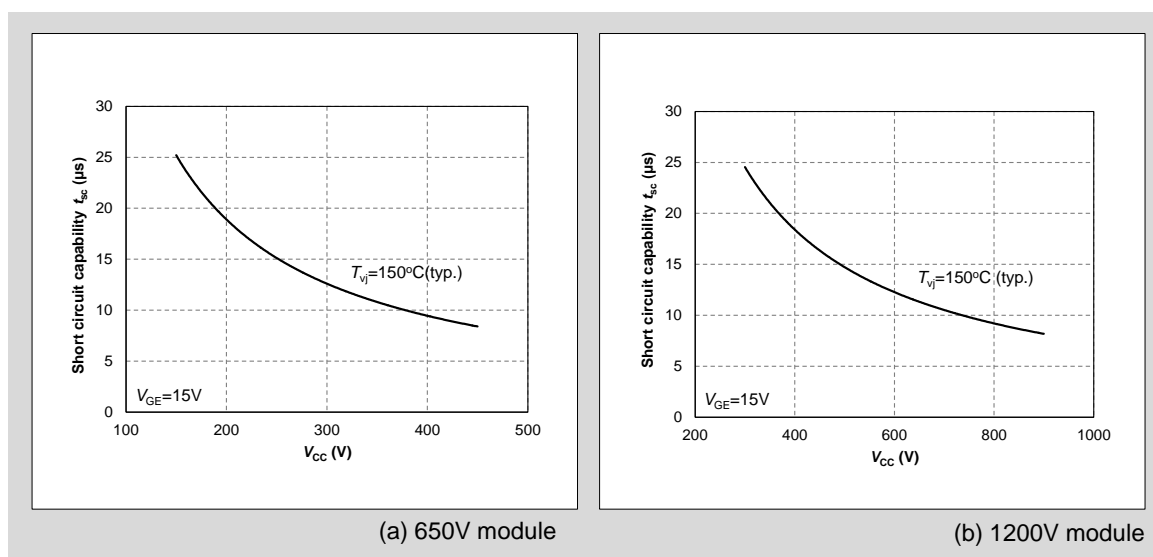


Fig.2-1 Short circuit capability of X-series IGBT modules as function of the applied voltage  $V_{CC}$  ( $V_{GE}=15V$ )

### 3. Overvoltage Protection and Safe Operating Area

#### 3.1 Overvoltage protection

Due to fast switching speed of IGBTs, a high  $di/dt$  is generated during the IGBT turn-off and the IGBT turn-on / FWD reverse recovery. This high  $di/dt$  causes a high overvoltage due to the external wiring stray inductance. If the overvoltage exceeds the module's maximum rated voltage ( $V_{CES}$ ), it can lead to the destruction of the module. There are several methods to avoid high overvoltage like adding a snubber circuit, adjusting the gate resistance  $R_G$ , or reducing the inductance of the main circuit.

Fig.2-2 shows a schematic diagram of turn-off and reverse recovery waveforms as well as the specific definition of overvoltage. The overvoltage which arises between collector and emitter during the IGBT turn-off is called  $V_{CEP}$ .  $V_{AKP}$  defines the overvoltage which occurs between the anode and the cathode of the FWD during the reverse recovery phase.

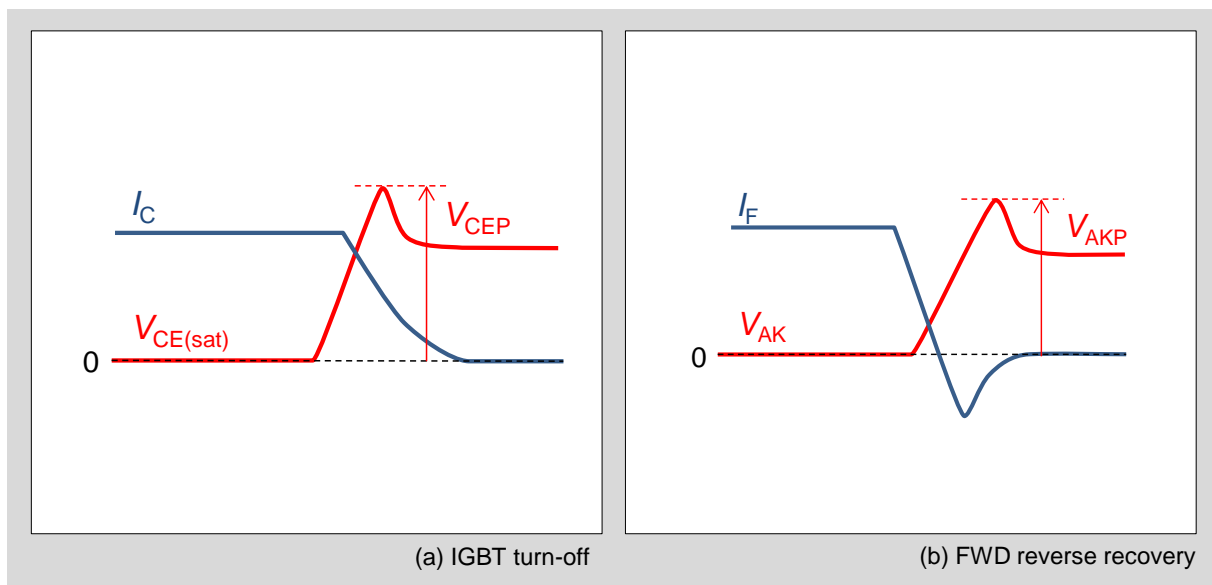


Fig.2-2 Schematic diagram of waveforms and overvoltages for (a) IGBT turn-off and (b) FWD reverse recovery

The overvoltage characteristics are described below using the following two modules serving as example: 7MBR100XRA065-50 (650V/100A) X-series and 7MBR100XNA120-50 (1200V/100A) X-series.

Fig.2-3 shows an example of the relation between the main circuit stray inductance ( $L_s$ ) and the overvoltage  $V_{CEP}$  when the IGBT is switched off. It is obvious that  $V_{CEP}$  increases with increasing  $L_s$ . Due to this coherence, the main circuit has to be designed with the lowest possible inductance. Fuji recommends the use of laminated bus bars for reducing the external inductance value.

Fig.2-4 shows an example of the relation between the applied voltage  $V_{CC}$  and the overvoltage  $V_{AKP}$  and  $V_{CEP}$ . As one can easily see from this figure, by increasing  $V_{CC}$  the overvoltage  $V_{CEP}$  and  $V_{AKP}$  will increase as well.

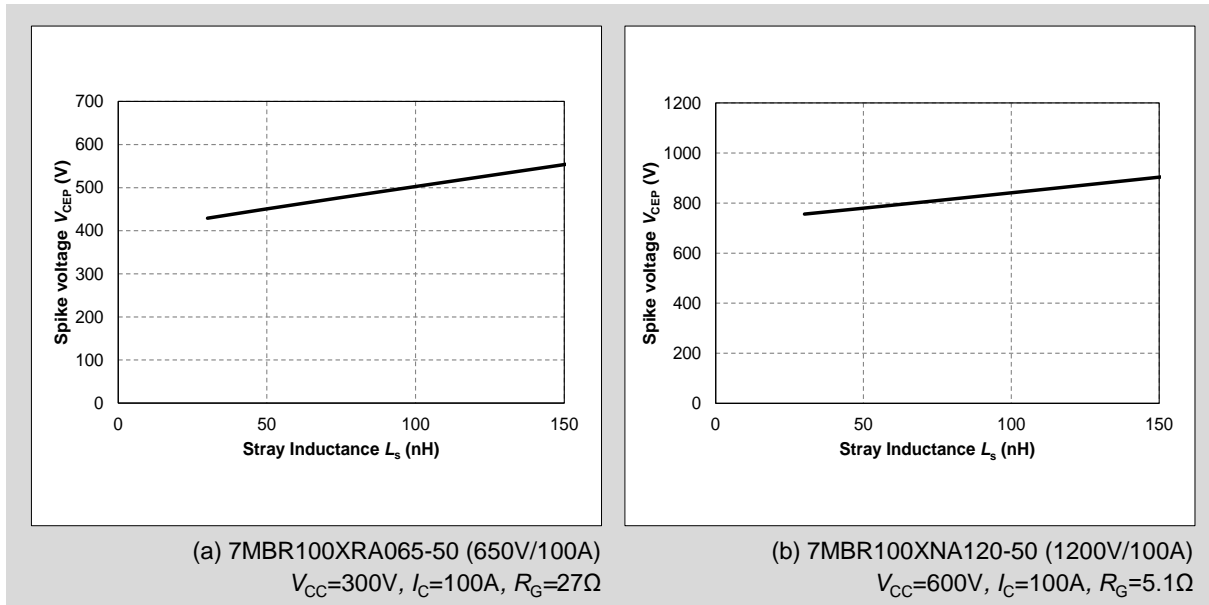


Fig.2-3 Example of the relation between stray inductance  $L_s$  and IGBT turn-off overvoltage

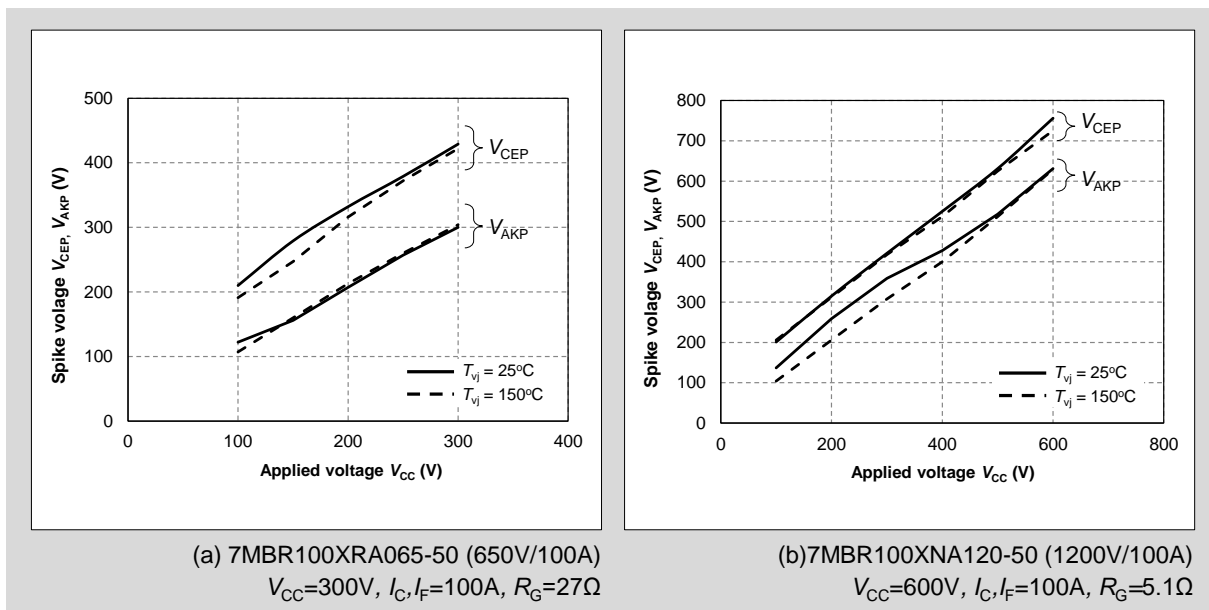


Fig.2-4 Example of the relation between the applied voltage  $V_{CC}$  and the overvoltage in IGBT turn-off and FWD reverse recovery

Fig.2-5 shows an example of the relation between the  $I_C$  and the overvoltage  $V_{CEP}$  and relation between  $I_F$  and  $V_{AKP}$ , respectively.  $V_{CEP}$  is increasing with increasing  $I_C$ . On the other hand,  $V_{AKP}$  tends to be larger for smaller values of the  $I_F$  currents. The largest value for  $V_{AKP}$  occurs for values smaller than one tenth of the rated current. During design phase it is therefore necessary to evaluate and take into account the overvoltage for the actual used current.

Fig.2-6 shows an example of the relation between the gate resistance  $R_G$  and the overvoltage  $V_{AKP}$ .

In each subfigure two curves are displayed. One represents the rated current 100A and the other one represents one tenth of the rated current, 10A. It has to be highlighted that  $V_{AKP}$  is increasing with decreasing  $R_G$  and  $I_F$  values.

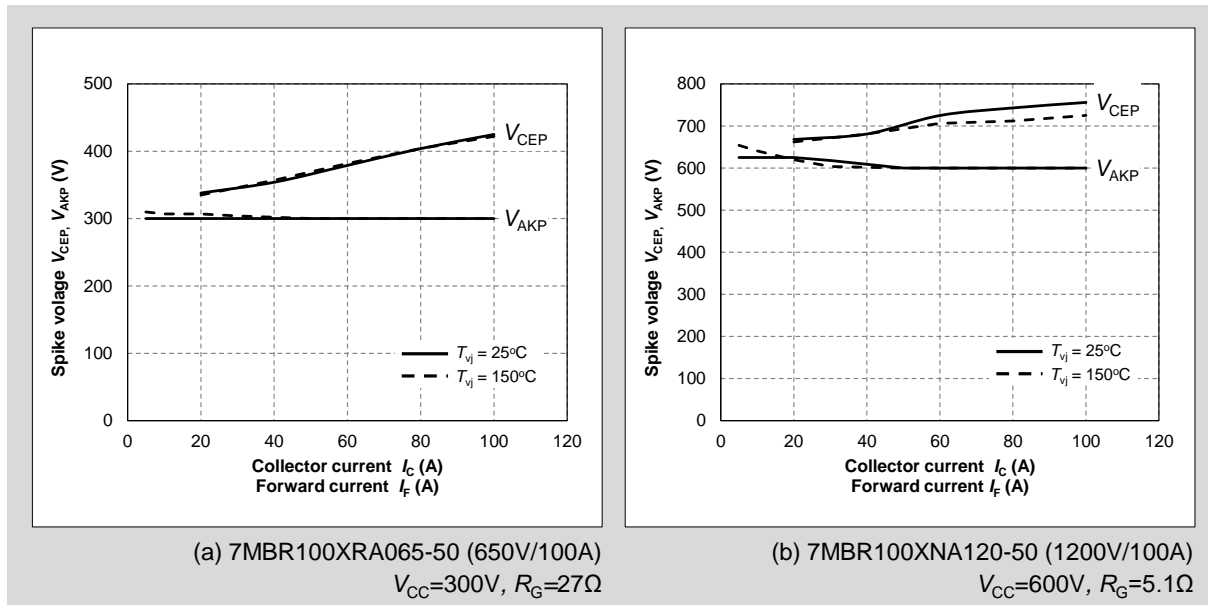


Fig.2-5 Example of the relation between  $I_C$  and overvoltage  $V_{CEP}$  and  $I_F$  and overvoltage  $V_{AKP}$

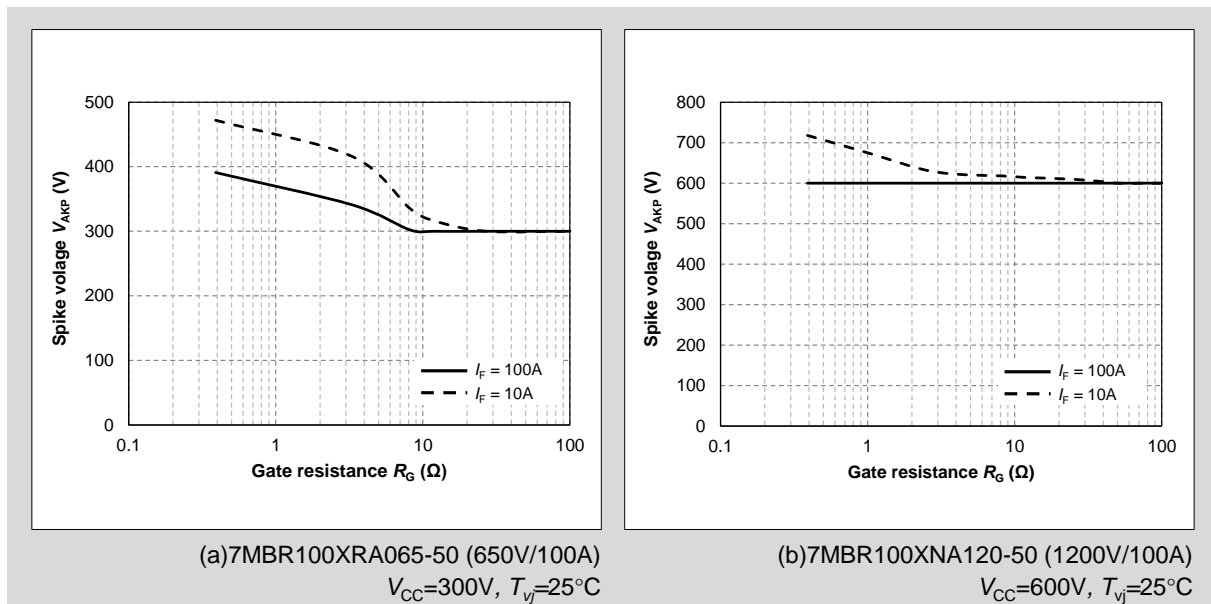


Fig.2-6 Example of the relation between gate resistance and overvoltage  $V_{AKP}$  of FWD reverse recovery

As described above, the value of the overvoltage generated in IGBT modules varies greatly depending on the used driving conditions, main circuit stray inductance  $L_s$  and the switching conditions.



Besides this, external parts like snubber circuits, capacitor values and gate drive capability also have an influence on the overvoltage.

When using IGBT modules, please make sure that the overvoltage will stay within the Reverse Bias Safety Operating Area (RBSOA) for all operating conditions in all various equipment such as inverter systems where the IGBT will be used in. If the overvoltage exceeds the guaranteed RBSOA, please take countermeasures like changing the gate resistance, reducing the stray inductance or adding a snubber circuit. In addition, it could be appropriate to use different gate resistances for turn-on and turn-off in order to optimize the driving condition.

### 3.2 Gate resistance influence on overvoltage during turn-off

In order to properly design the overvoltage protection, Fig.2-7 shows the relation between the gate resistance  $R_G$  value and the turn-off overvoltage  $V_{CEP}$  for X-series 1200V IGBT module.

Be aware that the IGBT modules belonging to the 4<sup>th</sup> generation (S-series) or even older ones show a different relation. In order to suppress the overvoltage usually an increase of  $R_G$  has been a suitable countermeasure. Now, since the carrier injection efficiency has been improved starting with 5<sup>th</sup> generation (U-series) the general relation between  $R_G$  and the overvoltage has been changed.

Due to this change increasing  $R_G$  value may cause now increasing overvoltage  $V_{CEP}$  values in contrary to the behavior of old generation products. Therefore, please select the gate resistance value carefully during the design phase to match the requirements and parameters of the actual device where the IGBT module will be used in.

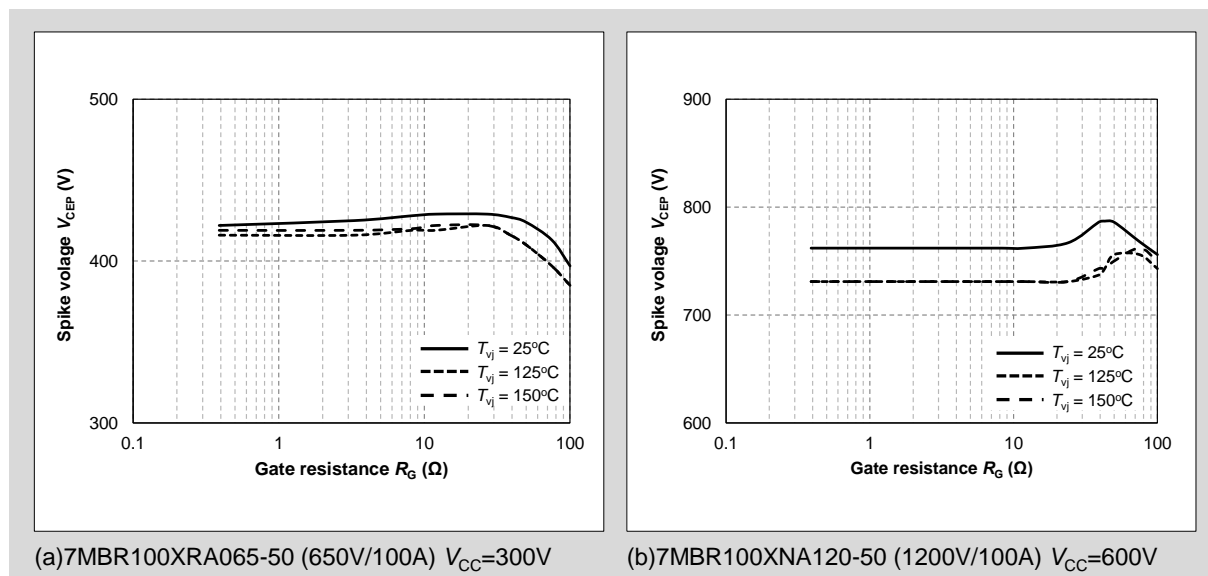


Fig.2-7 Example of the relation between gate resistance  $R_G$  and turn-off overvoltage  $V_{CEP}$

#### Reference

- 1) Y. Onozawa et al., "Investigation of carrier streaming effect for the low spike fast IGBT turn-off", Proc. ISPSD, pp. 173-176, 2006.

### 3.3 Overvoltage Protection under short circuit condition

When a short circuit occurs, the  $I_C$  sharply increases. In this case a larger  $I_C$  has to be cut off compared to a normal operation during turn-off. Thus, there is an additional RBSOA (Reverse Bias Safe Operating Area) for non-repetitive pulse is defined for the short circuit condition.

Fig.2-8 shows RBSOA (repetitive pulse) and RBSOA (non-repetitive pulse) for the 650V and 1200V 7<sup>th</sup> generation X-series modules. The  $V_{CE}-I_C$  locus has to stay within the RBSOA (non-repetitive pulse) during a short circuit condition until it will be turned off. Unless stated otherwise the voltage  $V_{CE}$  of RBSOA is the voltage measured at the main terminals of the module.

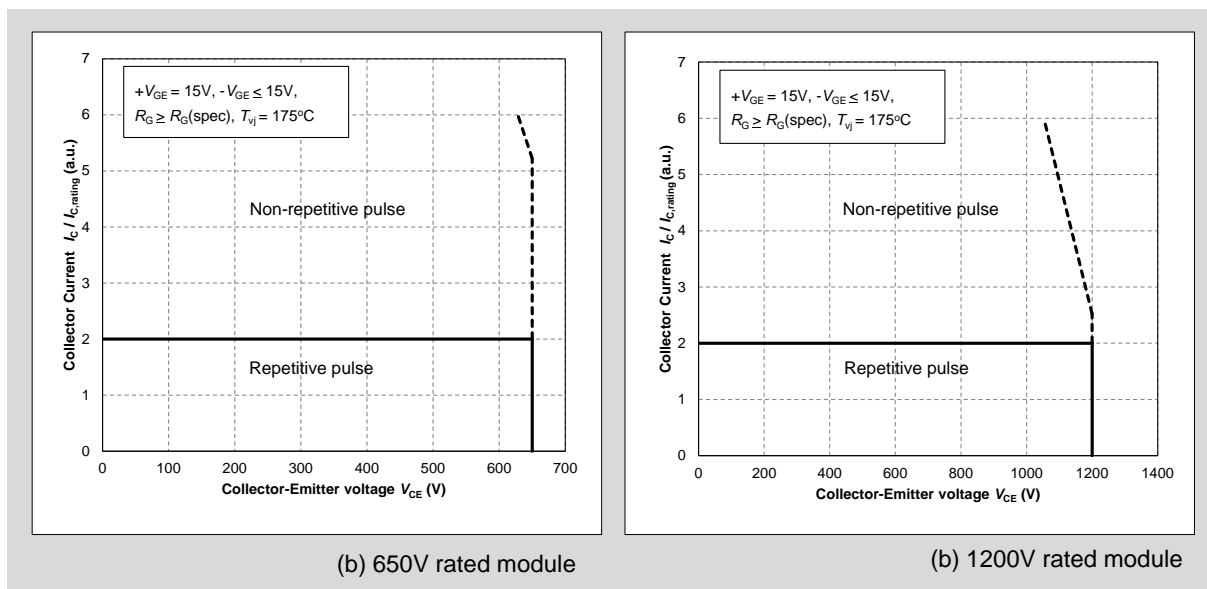


Fig.2-8 RBSOA for IGBT

### 3.4 Safe Operating Area for FWD

In the design phase, SOA (Safe Operating Area) for FWD, which exists similar to RBSOA for IGBT, has to be carefully considered. As shown in Fig.2-9 the SOA for FWD is indicated as the area which is limited by the maximum power ( $P_{max}$ ) during reverse recovery. The maximum power is defined as the product of current  $I_F$  and voltage  $V_{AK}$ . Therefore, it is mandatory to ensure that the  $V_{AK}-I_F$  locus of the FWD always stays within the SOA. Unless stated otherwise the voltage  $V_{AK}$  of SOA is the voltage measured at the main terminals of the module.

Fig.2-9 shows an example of SOA for the FWD for 2MBI600XNE120-50 (600A/1200V). In this case,  $P_{max}$  is given as 420 kW.

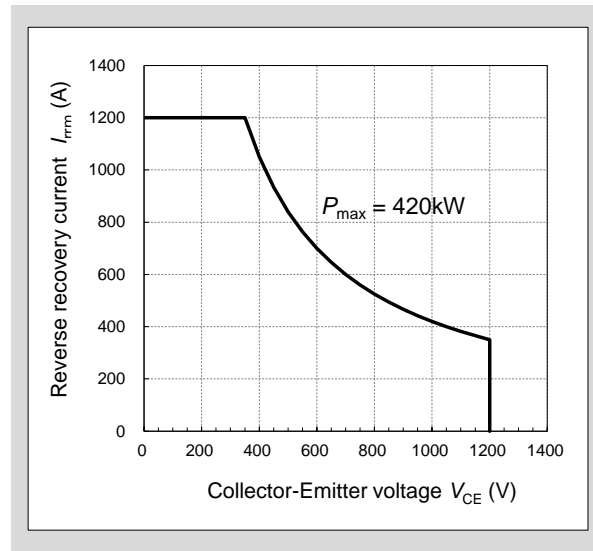


Fig.2-9 Example of Safe Operating Area (SOA) for FWD

An example of the reverse recovery waveform is shown in Fig.2-10(a) whereas in Fig.2-10(b) SOA for FWD including  $V_{AK}$ - $I_F$  locus for the reverse recovery waveforms from Fig 2-10(a) are displayed. The blue line in the latter figure represents the  $V_{AK}$ - $I_F$  locus resulting from a circuit using a snubber circuit. The locus is within the SOA for FWD and the circuit will not cause any problem. The red line in the same figure represents a  $V_{AK}$ - $I_F$  locus which is exceeding the SOA for the FWD. Hence, the used circuit may lead to the destruction of the FWD. In consequence it is mandatory to take appropriate action for keeping the locus within the SOA. For instance, this might be achieved by using a larger gate resistance for the IGBT.

The gate driving condition must be defined and chosen in order to keep the  $V_{AK}$ - $I_F$  locus within the SOA for FWD for all operating conditions and all used devices.

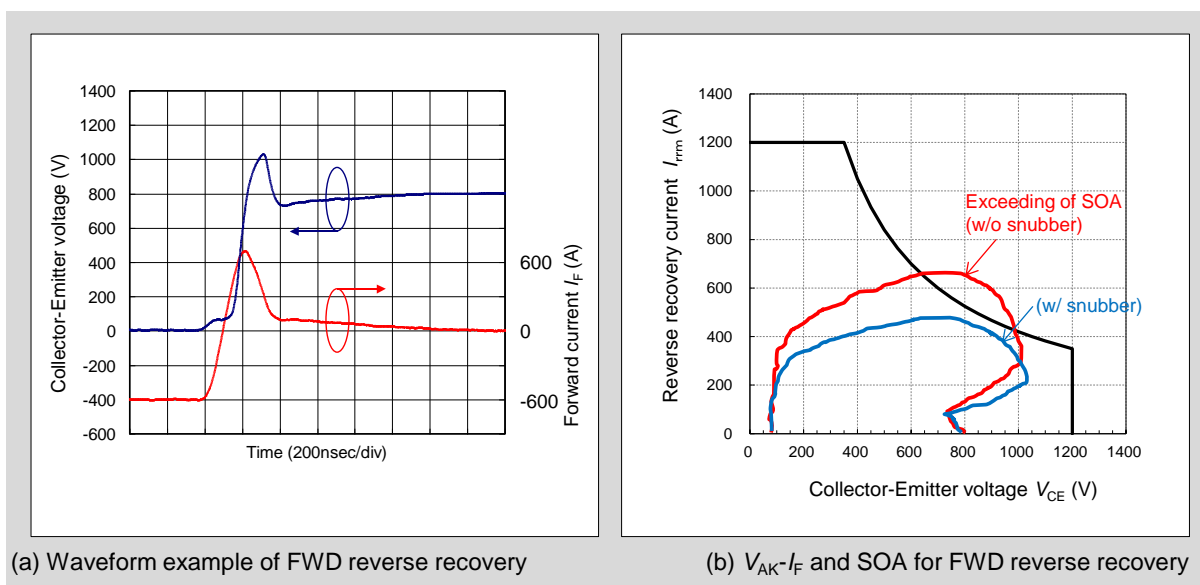


Fig.2-10 Reverse recovery waveform and  $V_{AK}$ - $I_F$  locus for FWD reverse recovery

## 4. Parallel Connection

IGBT modules can be connected in parallel for increasing the current capability. This chapter describes the parameters which have to be taken into account when X-series IGBT modules are going to be connected in parallel.

### 4.1 Junction temperature dependency of output characteristics and current imbalance

The  $T_{vj}$  dependence of output characteristics influences the current imbalance of modules which are connected in parallel significantly. Fig.2-11 shows typical output characteristic of 7<sup>th</sup> generation X-series IGBT modules ( $V_{CE(sat)}$ - $I_C$  relation). As shown in Fig.2-11, the X-series IGBT has a positive temperature coefficient which means that increasing  $T_{vj}$  leads to larger  $V_{CE(sat)}$  values. Due to the positive temperature coefficient the current imbalance will be automatically regulated because the collector current  $I_C$  will decrease when  $T_{vj}$  increases.

As all output characteristics have a positive junction temperature coefficient, the X-series IGBT modules have suitable characteristics for parallel operation. According to historical data the positive temperature coefficient has been achieved by Fuji Electric starting from the 4<sup>th</sup> IGBT generation (S-series).

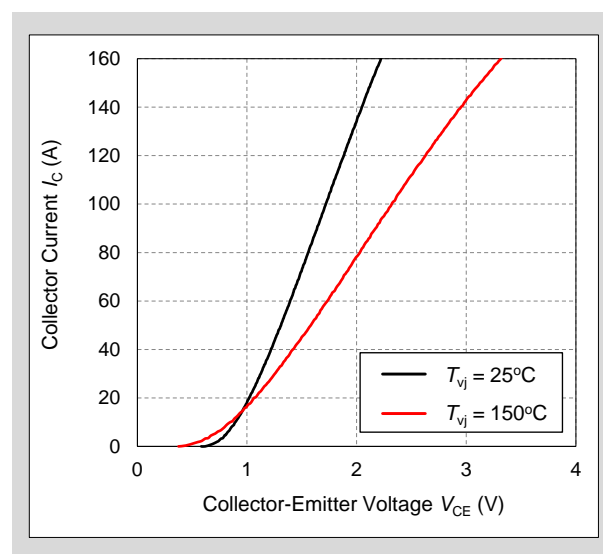


Fig.2-11 Relation between  $T_{vj}$  (1200V/100A) and IGBT output characteristics

### 4.2 $V_{CE(sat)}$ variation and current imbalance

The ratio of current sharing between IGBT modules in parallel connection is called current imbalance ratio  $\alpha$ . This ratio is determined by the variation of  $V_{CE(sat)}$  of the IGBT itself and the junction temperature dependency of the output characteristics.

The relation between the current imbalance ratio  $\alpha$  and variation  $\Delta V_{CE(sat)}$  of  $V_{CE(sat)}$  for two X-series IGBT modules connected in parallel are shown in Fig.2-12. The current imbalance ratio  $\alpha$  is obtained by applying Equation 2-1 with  $I_{C1}$  as current value and  $I_{C(ave)}$  ( $=I_{C1}/2+I_{C2}/2$ ) as the average current of the two paralleled modules.

As shown in Fig.2-12, an increase of  $\Delta V_{CE(sat)}$  results in a larger current imbalance  $\alpha$ . Hence, parallel connection of modules requires a combination of modules which have only slightly different  $V_{CE(sat)}$  values.

$$\alpha = \left( \frac{I_{C1}}{I_{C(ave)}} - 1 \right) \times 100 \quad \text{Equation 2-1}$$

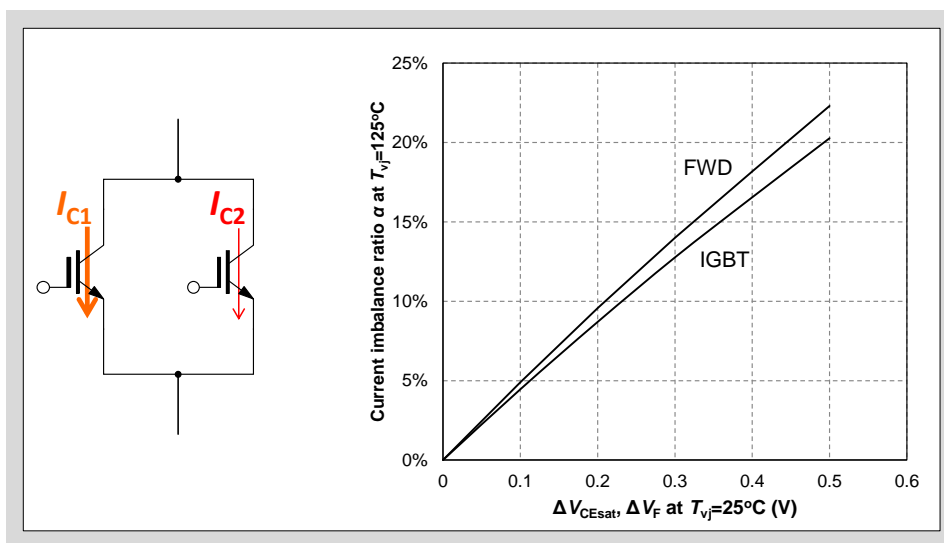


Fig.2-12  $V_{CE(sat)}$  and  $V_F$  variation and current imbalance ratio (1200V)

## 5. Mounting Instruction

Please refer to the WEB site (see URL below) and download the suggested mounting instruction for the concerned package of X-series module.

Fuji Electric Power Semiconductor - Design Support

<http://www.fujielectric.com/products/semiconductor/model/igbt/mounting/index.html>